



(University of Choice)

**MASINDE MULIRO UNIVERSITY OF  
SCIENCE AND TECHNOLOGY  
(MMUST)**

**MAIN CAMPUS**

**UNIVERSITY EXAMINATIONS  
2021 / 2022 ACADEMIC YEAR**

**THIRD YEAR SECOND SEMESTER EXAMINATIONS**

**FOR THE DEGREE  
OF  
BACHELOR OF SCIENCE IN ELECTRICAL AND  
COMMUNICATION ENGINEERING**

**COURSE CODE: ECE 323**

**COURSE TITLE: NETWORK ANALYSIS AND SYNTHESIS**

**DATE: WEDNESDAY, APRIL, 27<sup>TH</sup>, 2022. TIME: 3:00 – 5:00 PM**

---

**INSTRUCTIONS TO CANDIDATES**

Answer Question ONE (1) and ANY OTHER TWO (2) Questions  
Scientific calculators may be used

MMUST observes ZERO tolerance to examination cheating

This Paper Consists of 6 Printed Pages. Please Turn Over.



**QUESTION ONE**

**[30Marks]**

(a) A DC voltage of 20 V is applied in an  $R$ - $L$  circuit where  $R = 5\Omega$  and  $L = 10$  H. Determine;

- (i) the current  $i$ ; [3marks]
- (ii) voltage across resistor and voltage across the inductor; [3marks]
- (iii) the maximum value of stored energy [3marks]

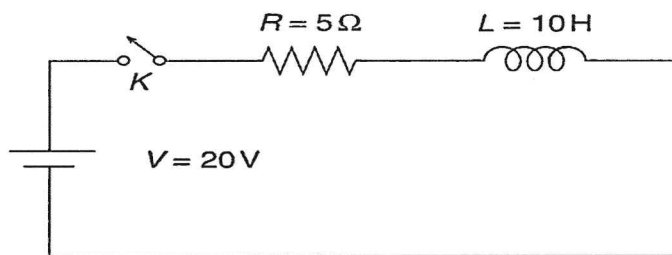


Figure Q1(a)

(b) Determine the time domain current response  $i(t)$  of the circuit shown in Figure Q1(b) using Laplace transforms. [5marks]

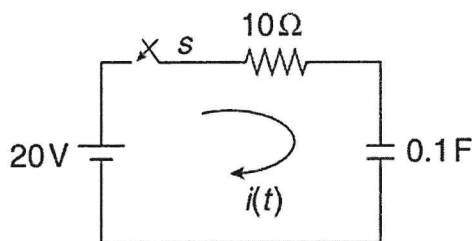


Figure Q1(b)

(c) Given a two-port network in figure Q1(c), determine its  $Z$ -parameters. [6marks]

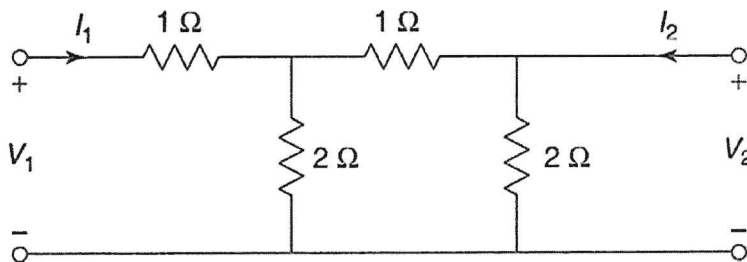


Figure Q1(c)

(d) Test whether the polynomial  $P(s) = s^3 + 4s^2 + 5s + 2$  is Hurwitz [4marks]

(e) Draw the pole-zero plot of the following functions

- (i)  $F(s) = \frac{s(s+2)}{(s+1)(s+3)}$  [3marks]

$$(ii) V(s) = \frac{2s^2 + 80s + 1000}{s(s+10)(s+30)}$$

[3marks]

**QUESTION TWO**

**[20marks]**

(a) Determine the Z-parameters of the network given in Figure Q2(a) [6marks]


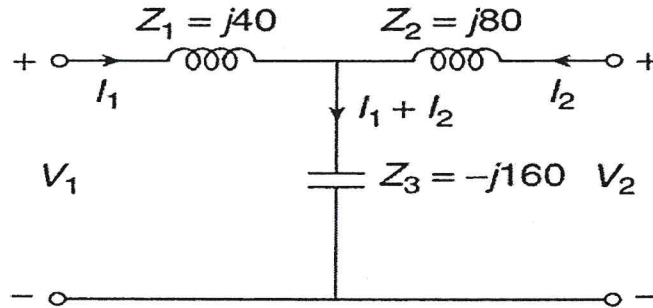


Figure Q2(a)

(b) (i) The admittance parameters of a pi network are  $Y_{11} = 0.09$  mho,  $Y_{12} = Y_{21} = 0.05$  mho and  $Y_{22} = 0.07$  mho. Determine the values of  $R_a$ ,  $R_b$  and  $R_c$ .

[4marks]

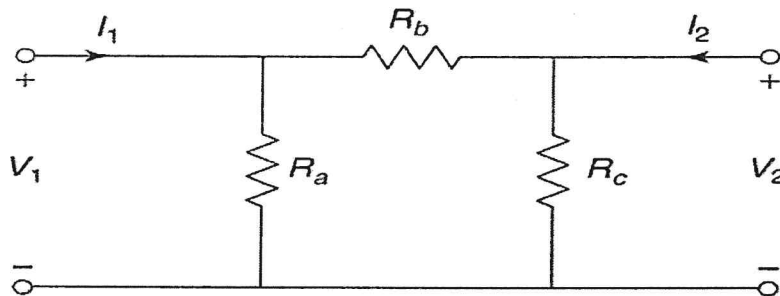

(ii) Synthesize the impedance function  $Z(s) = \frac{s^3 + 4s}{s^2 + 2}$  [4marks]

(iii) Realize the Cauer forms of the impedance function [6marks]

$$Z(s) = \frac{4(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

**QUESTION THREE**

**[20marks]**

(a) (i) Determine the poles and zeros of the impedance of the network shown in shown in Figure Q3(a) and plot them on the s-plane [4marks]




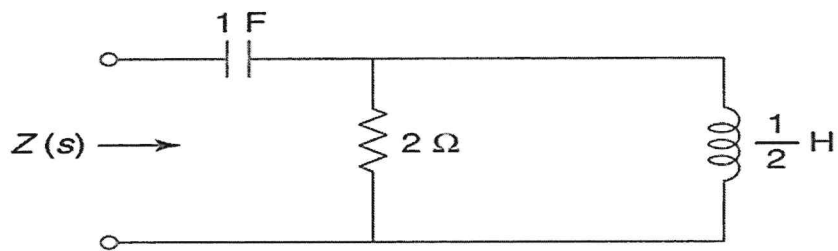


Figure Q3(a)

(ii) Determine transmission (ABCD) parameters for the network

[4marks]

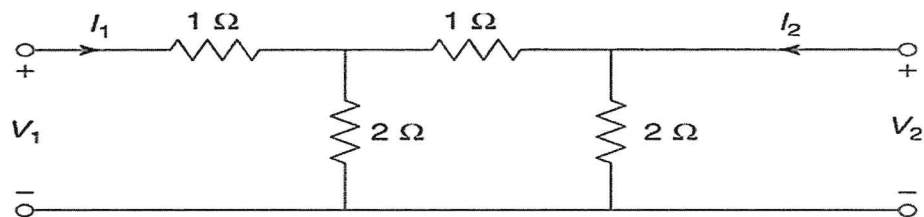

(b) Determine the Y-parameters for the network shown in Figure Q3(b)

[4marks]


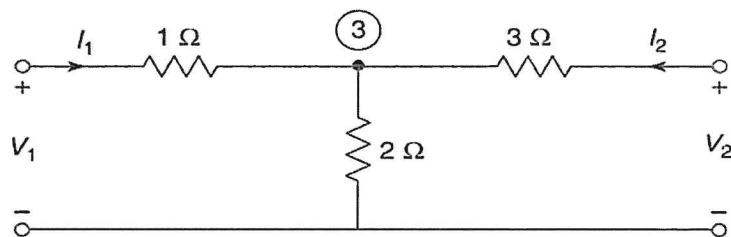


Figure Q3(b)

(c) Two identical sections of the network shown in Figure Q3 (c) are connected in series. Obtain Z-parameters of the overall connection. Determine the transmission parameters of the overall connection.

[4marks]

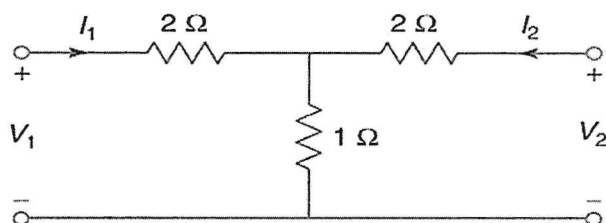

(ii)  $V(s) = \frac{2s^2 + 80s + 1000}{s(s+10)(s+30)}$

[3marks]

**QUESTION TWO**

**[20marks]**

(a) Determine the Z-parameters of the network given in Figure Q2(a)[6marks]


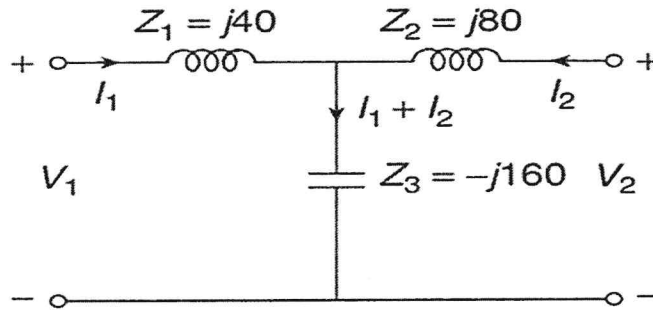


Figure Q2(a)

(b) (i) The admittance parameters of a pi network are  $Y_{11} = 0.09$  mho,  $Y_{12} = Y_{21} = 0.05$  mho and  $Y_{22} = 0.07$  mho. Determine the values of  $R_a$ ,  $R_b$  and  $R_c$ .

[4marks]

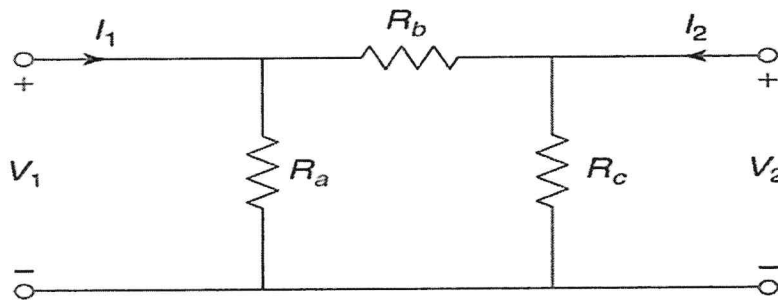

(ii) Synthesize the impedance function  $Z(s) = \frac{s^3 + 4s}{s^2 + 2}$

[4marks]

(iii) Realize the Cauer forms of the impedance function

[6marks]

$$Z(s) = \frac{4(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

**QUESTION THREE**

**[20marks]**

(a) (i) Determine the poles and zeros of the impedance of the network shown in shown in Figure Q3(a) and plot them on the s-plane [4marks]

Figure Q3 (c)

(d) The Z-parameters of a two port network are;  $Z_{11}=10\Omega$ ,  $Z_{12}=Z_{21}=5\Omega$ ,  $Z_{22}=20\Omega$ . Determine the equivalent T-network. [4marks]

**QUESTION FOUR**

**[20marks]**

(a) A circuit has resistance of  $1000\Omega$  and a series capacitance of  $0.1 \mu\text{F}$ . At  $t=0$ , it is connected to a  $12 \text{ V}$  battery as shown in Figure Q4(a). Determine;

- i. The current at  $t = 0$  [2marks]
- ii. Rate of change of current at  $t = 0$  [2marks]
- iii. Rate of change of capacitor voltage at  $t = 0$  [2marks]
- iv. Current at  $t = 0.1 \text{ ms}$  [2marks]
- v. Voltage across capacitor at  $0.1 \text{ ms}$  [2marks]

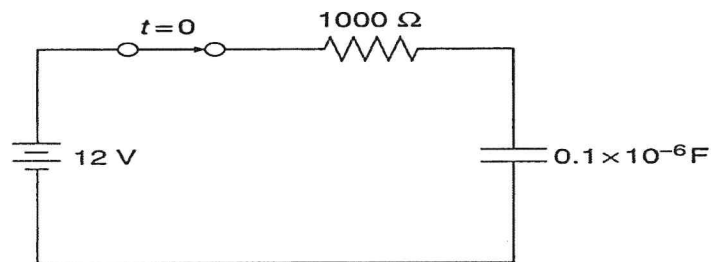


Figure Q4(a)

(b) Determine the current flowing in the circuit of Figure Q4(b) using the following methods.

- (i) Differential equation [4marks]
- (ii) Laplace transform [4marks]

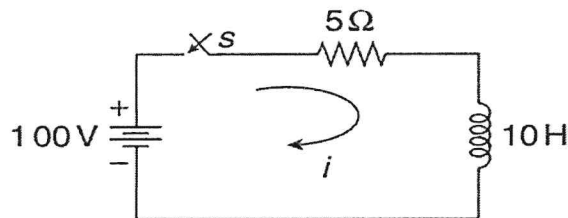


Figure Q4(b)

(c) Realize the Foster Forms of the impedance function [8marks]

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$$

**QUESTION FIVE**

**[20marks]**

(a) Determine hybrid parameters for the network of Figure Q5(a) [8marks]

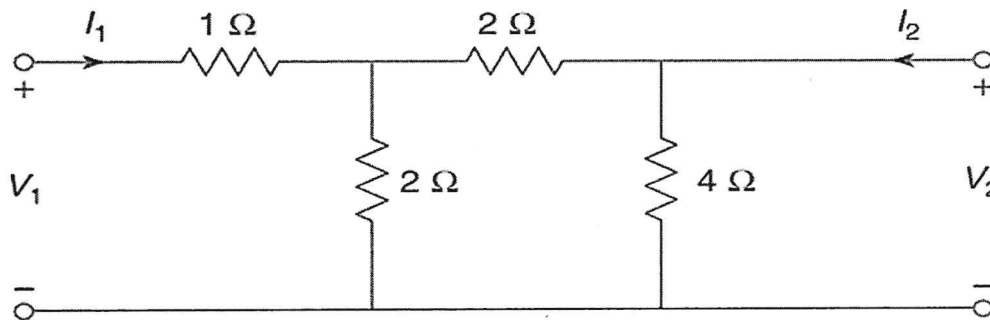


Figure Q5(a)

(b) Realize networks having the following functions

(i)  $Z(s) = \frac{s^2+2s+10}{s(s+5)}$  [4marks]

(ii)  $Z(s) = \frac{6s^3+5s^2+6s+4}{2s^3+2s}$  [4marks]

(iii)  $Y(s) = \frac{4s^2+6s}{s+1}$  [4marks]

**Appendix**

**Table 1: Expression of Two-Port Parameters**

Name	Express	In terms of	Defining equations
Impedance	$V_1, V_2$	$I_1, I_2$	$V_1 = z_{11}I_1 + z_{12}I_2$ and $V_2 = z_{21}I_1 + z_{22}I_2$
Admittance	$I_1, I_2$	$V_1, V_2$	$I_1 = y_{11}V_1 + y_{12}V_2$ and $I_2 = y_{21}V_1 + y_{22}V_2$
Hybrid	$V_1, I_2$	$I_1, V_2$	$V_1 = h_{11}I_1 + h_{12}V_2$ and $I_2 = h_{21}I_1 + h_{22}V_2$
Transmission	$V_1, I_1$	$V_2, -I_2$	$V_1 = AV_2 - BI_2$ and $I_1 = CV_2 - DI_2$