



(University of Choice)

**MASINDE MULIRO UNIVERSITY OF
SCIENCE AND TECHNOLOGY
(MMUST)**

MAIN CAMPUS

**UNIVERSITY EXAMINATIONS
2021 / 2022 ACADEMIC YEAR**

SECOND YEAR SECOND SEMESTER EXAMINATIONS

**FOR DIPLOMA
IN
ELECTRICAL AND ELECTRONICS ENGINEERING**

COURSE CODE: DEE 073

COURSE TITLE: ELECTRONICS II

DATE: Wednesday 20th April, 2022

TIME: ~~12.00 p.m - 2.00 p.m~~ 8.00 AM - 10.00 AM

INSTRUCTIONS TO CANDIDATES

ANSWER ALL QUESTIONS IN SECTION A AND TWO QUESTIONS IN SECTION B.
TIME: 2 Hours

MMUST observes ZERO tolerance to examination cheating


This Paper Consists of 3 Printed Pages. Please Turn Over. 

MASINDE MULIRO UNIVERSITY OF SCIENCE & TECHNOLOGY

DEE 073: Electronics II

SECTION A (30 MARKS): Answer ALL questions

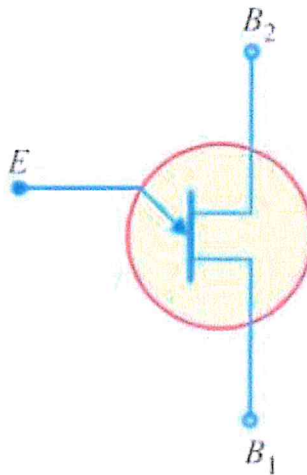1. With reference to an amplifier, define the following terms:
 - i) Amplification (1 mk)
 - ii) Gain (1 mk)
 - iii) Bandwidth (1 mk)
2. An amplifier is rated at 12V, 50Hz with an input power of 20W. The output power and voltage is 16000W and 236V respectively. Calculate:
 - a) Power gain in dB (2 mks)
 - b) Voltage gain in dB (2 mks)
 - c) Current gain in dB (2 mks)
3. Define an operational amplifier. (2 mks)
4. Define the following terms with respect to op-amps:
 - i) Slew rate (2 mks)
 - ii) Common mode rejection ratio (CMRR) (2 mks)
5. Explain the concept of virtual ground in op-amps. (4 mks)
6. State FIVE characteristics of an ideal op-amp. (5 mks)
7. a) The figure below shows the symbol of a semiconductor device. Explain its operation. (4 mks)



- b) The intrinsic stand-off ratio for a UJT is 0.6 and the inter-base resistance is $10\text{k}\Omega$. Determine the values of r_{B1} and r_{B2} . (2 mks)

SECTION B: Answer any TWO questions

8. a) With the aid of an appropriate circuit diagram, explain how a transistor can be used to amplify a signal. (10 mks)
- b) Derive the h-parameter current gain equation for a transistor amplifier. (10 mks)
9. a) Define a tuned amplifier. (1 mk)
- b) A parallel resonant circuit has a capacitor of 250pF in one branch and inductance of 1.25mH plus a resistance of 10Ω in the parallel branch.
Find:
- i) resonant frequency (3 mks)
 - ii) impedance of the circuit at resonance (3 mks)
 - iii) Q-factor of the circuit. (3 mks)
- c) Explain why tuned circuits are not used for low frequency amplification. (4 mks)
- d) Draw the circuit of a double tuned amplifier and hence its frequency response curve. (6 mks)
10. a) Define a multivibrator. (1 mk)
- b) Using an appropriate diagram, explain the operation of a transistor monostable multivibrator. (10 mks)
- c) In a differentiating circuit, $R = 10\text{ k}\Omega$ and $C = 2.2\ \mu\text{F}$. If the input voltage goes from 0 V to 10 V at a constant rate in 0.4 s, determine the output voltage. (4 mks)
- d) Using a relevant circuit diagram and waveforms, explain the operation of a positive clipper. (5 mks)