



(University of Choice)  
**MASINDE MULIRO UNIVERSITY OF  
SCIENCE AND TECHNOLOGY  
(MMUST)**

**MAIN CAMPUS**

**UNIVERSITY EXAMINATIONS  
2021/2022 ACADEMIC YEAR**

**FIRST YEAR SECOND SEMESTER EXAMINATIONS**

**FOR THE DEGREE  
OF  
BACHELOR OF SCIENCE IN RENEWABLE ENERGY TECHNOLOGY**

**COURSE CODE: ECE 102**

**COURSE TITLE: CIRCUIT THEORY**

**DATE: Monday, April 25<sup>th</sup>, 2022 TIME: 3.00 - 5.00 PM**

---

**INSTRUCTIONS TO CANDIDATES**

Answer Question ONE and any other TWO (2) questions

Marks will be awarded for correct working even if the answer is wrong

**MMUST observes ZERO tolerance to examination cheating**

This Paper Consists of 7 Printed Pages. Please Turn Over.



**SECTION A**

**Question one**

- What is a source as used in electrical circuits? List any two types of electrical sources commonly used. (4mks)
- With aid of diagrams differentiate between dependent and independent electrical sources. (5mks)
- State two applications where the compensation theorem is particularly useful to be applied. (2mks)
- From Figure 1D compute the ratio of  $i_1/i$ . (5mks)

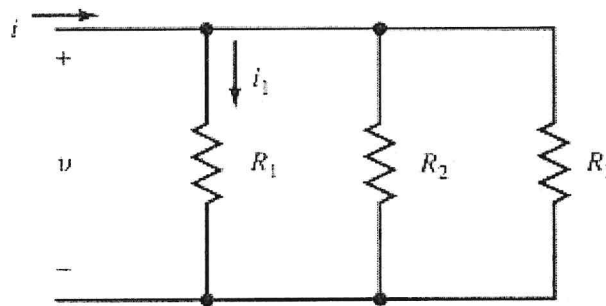


Figure 1D

- List and briefly explain three important terms associated with an alternating quantity. (4.5mks)
- Define the RMS value of an alternating quantity and give the RMS expressions for current. (3mks)
- A parallel circuit comprises of a resistor of  $20\Omega$  in series with an inductive reactance  $15\Omega$  in one branch and a resistor of  $30\Omega$  in series with a capacitive reactance of  $20\Omega$  in the other branch as in Figure 1G. Determine the current and power dissipated in each branch if the total current drawn by the parallel circuit is  $10\angle-30^\circ\text{A}$ . (6.5mks)

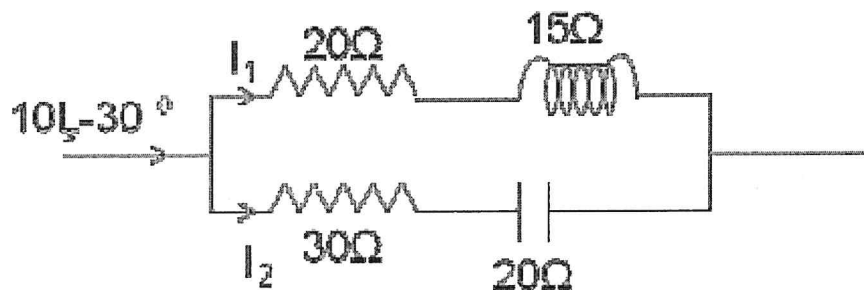


Figure 1G

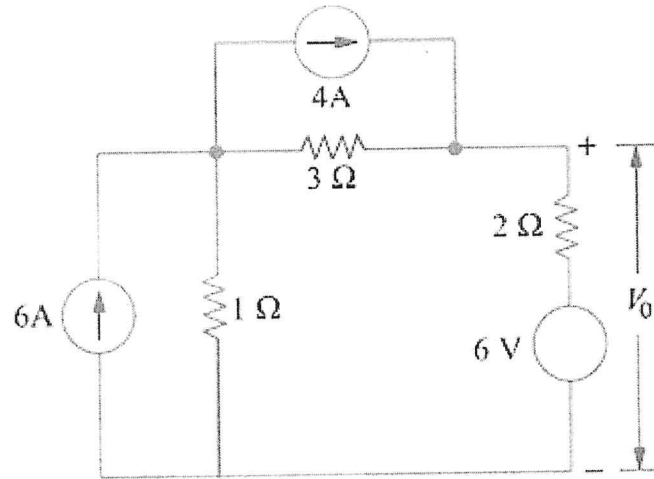


Figure 2C.

**Question three**

- a) State two applications where the compensation theorem is particularly useful to be applied. (4mks)
- b) Calculate the values of new currents in the network illustrated in Figure 3B when the resistor  $R_3$  is increased by 30%. (8mks)

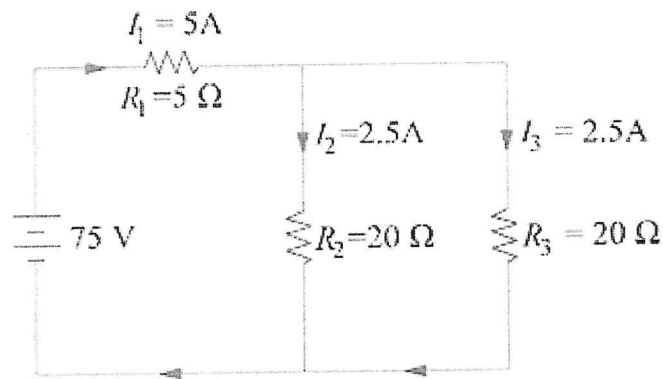


Figure 3B.

- c) Calculate the currents in the various branches of the network shown in Figure 3C and then utilize the principle of Superposition and Reciprocity theorem together to find the value of the current in the 1-volt battery circuit when an e.m.f. of 2 volts is added in branch BD opposing the flow of original current in that branch. (8mks)

**Question five**

- a) From the circuit shown in Figure 5A derive the average power over one cycle. (5mks)

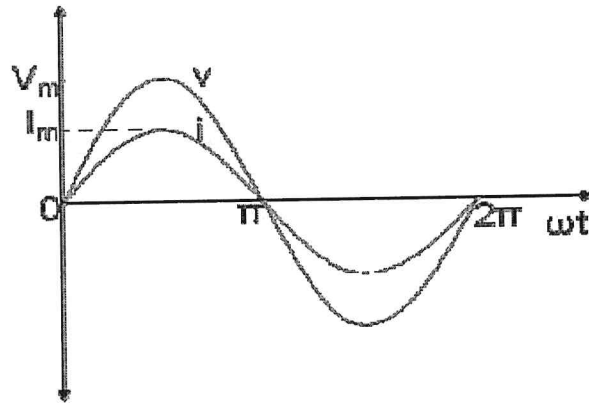


Figure 5A.

- b) For the circuit shown in Figure 5B determine the branch voltage and currents and power delivered by the source using mesh analysis. (9mks)

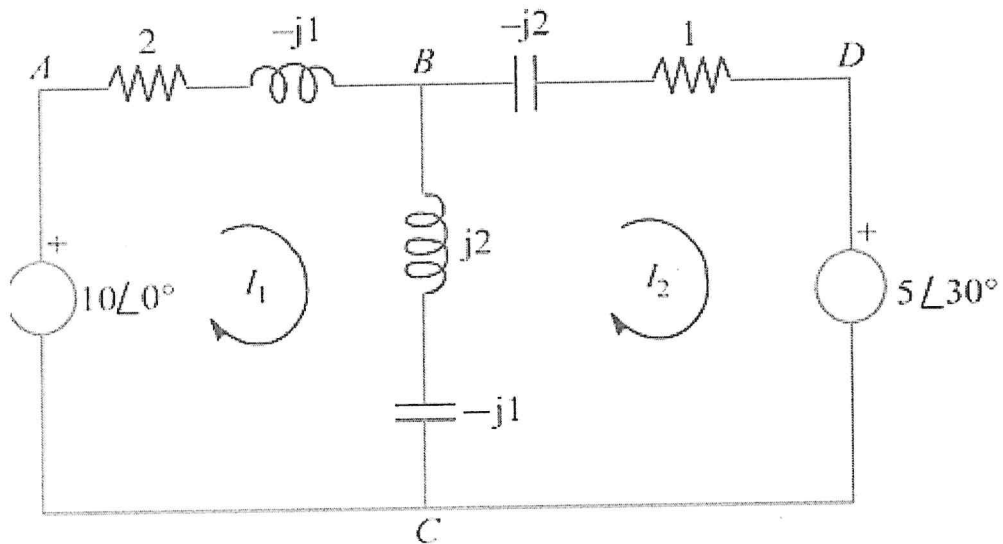


Figure 5B

- c) Use Nodal analysis to calculate the current flowing in each branch of the network shown in Figure 5C. (6mks)