



**MASINDE MULIRO UNIVERSITY OF
SCIENCE AND TECHNOLOGY
(MMUST)**

MAIN CAMPUS

**UNIVERSITY EXAMINATIONS
2021 / 2022 ACADEMIC YEAR**

SECOND YEAR SECOND SEMESTER EXAMINATIONS

**FOR THE DEGREE OF
BACHELOR OF SCIENCE
IN
MECHANICAL AND INDUSTRIAL ENGINEERING**

COURSE CODE: ECE 202

COURSE TITLE: ELECTRICAL MACHINES


DATE: Monday, April 25th 2022 Time: 12.00- 2.00pm

INSTRUCTIONS TO CANDIDATES

ANSWER QUESTION ONE AND ANY OTHER TWO QUESTIONS.
QUESTION ONE CARRIES 30 MARKS AND ALL OTHERS 20 MARKS EACH.

TIME: 2 Hours

MMUST observes ZERO tolerance to examination cheating

This Paper Consists of 4 Printed Pages. Please Turn Over. 

Question Two (20 marks)

- a) State two materials that can be used to make the brushes of a DC machine. [1 mark]
- b) Explain four advantages of paralleling DC generators. [4 marks]
- c) A shunt generator delivers 200 A at terminal voltage of 240V. The armature resistance and shunt field resistance are 0.01Ω and 80Ω respectively. The iron and friction losses equal 750W. Neglecting brush losses, find:
- i) emf generated,
 - ii) copper losses,
 - iii) output of the prime motor. [6 marks]
- d) Define the following terms:
- (i) critical speed, [1 mark]
 - (ii) critical field resistance. [1 mark]
- e) State and elaborate four losses that occur in a DC machine. [4 marks]
- f) Name and draw three characteristics of a DC shunt generator. [3 marks]

Question Three (20 marks)

- (a) Mention three tests performed on a transformer and state the losses that can be determined using these tests. [3 marks]
- (b) Define an ideal transformer. State three characteristics of an ideal transformer. [4 marks]
- (c) A 21.45-kVA, 3300/220-V distribution transformer is connected as a step-down autotransformer, with both the primary and secondary windings connected to the input and only the load connected to the secondary windings. *Draw a diagram* for this combination and determine:
- (i) the primary winding voltage,
 - (ii) the secondary winding voltage,
 - (iii) the ratio of transformation,
 - (iv) the nominal rating of the autotransformer. [6 marks]
- (d) (i) Mention four ways in which a three-phase transformer can be connected. [2 marks]
- (ii) A three-phase transformer which has a wye-delta connection is connected to a 12kV supply and draws a current of 10A. Considering the turns ratio of the transformer to be 12, determine:

- (i) the air-gap power P_2 ,
- (ii) the power converted P_m ,
- (iii) the output power P_{out} ,
- (iv) the efficiency of the motor.

marks]

[5