



(University of Choice)

**MASINDE MULIRO UNIVERSITY OF
SCIENCE AND TECHNOLOGY
(MMUST)**

MAIN CAMPUS

SUPPLEMENTARY/SPECIAL UNIVERSITY EXAMINATIONS

2021/2022 ACADEMIC YEAR

FOURTH YEAR SECOND SEMESTER EXAMINATIONS

**FOR THE DEGREE
OF
BACHELOR OF SCIENCE IN ELECTRICAL
AND
COMMUNICATION ENGINEERING**

COURSE CODE: ECE 424

COURSE TITLE: POWER ELECTRONICS II

DATE: OCTOBER 7TH, 2022 TIME: 3:00PM - 5:00PM

INSTRUCTIONS TO CANDIDATES

ANSWER QUESTION ONE AND ANY OTHER TWO QUESTIONS.
QUESTION ONE CARRIES 30 MARKS AND ALL OTHERS 20 MARKS EACH.

TIME: 2 Hours

MMUST observes ZERO tolerance to examination cheating

This Paper Consists of 4 Printed Pages. Please Turn Over. 

QUESTION ONE

1. A full-bridge inverter is operated from d.c. supply of 400 V and in a unipolar PWM mode. Determine:
 - a) Fundamental output voltage at $M = 0.5$
 - b) The first-five dominant harmonic order if $M = 12$.

[4 Marks]
2. Briefly explain why voltage control is necessary in inverter circuits and the various methods of voltage control in inverter circuits.

[4 Marks]
3. Discuss two (2) techniques applied to obtain variable d.c. voltage from a fixed d.c. voltage.

[4 Marks]
4. The single-phase half-bridge inverter has a resistive load of 5Ω and the center-tap dc input voltage is 12 V. Compute:
 - a) RMS value of the output voltage.
 - b) Fundamental component of the output voltage waveform.
 - c) Fundamental power consumed by the load.
 - d) The IGBT ratings
 - e) Total harmonic distortion THD
 - f) The distortion factor DF

[12 Marks]
5. Briefly highlight on three (3) converter classifications.

[6 Marks]

QUESTION TWO

1. In a table format, highlight the differences between circulating current and non-circulating current schemes of dual converters.

[2 Marks]
2. Design a dual converter to achieve at four-quadrant operation for $I_d = 10 A$ at 240 V. The converter is supplied from 420 V, three-phase and 50 Hz supply.

[8 Marks]
3. Consider a 20 HP, 240 V, 1200 rpm series motor whose combined field and armature resistance is 0.25Ω . Motor constants are $K_{af} = 0.03 Nm A^2$ and $K_{res} = 0.0075 Vsrad^{-1}$. The supply voltage is 240 V. Assuming a continuous and ripple free motor current, determine the following:
 - a) Motor torque
 - b) Motor current
 - c) Supply power factorFor the case in which the motor is controlled by a single-phase
 - i. Semiconverter
 - ii. Full converter

[10 Marks]

QUESTION THREE

1. For a three-phase bridge inverter operating in 120° conduction mode, determine:
 - a) The dc voltage for a fundamental line voltage of 415 V
 - b) The rms line and phase voltage
 - c) The device voltage rating.

[6 Marks]
2. A three phase six-pulse, 55 kVA, 415 V cycloconverter is operating at a firing angle of 60° and supplying load of 0.9 power factor. Determine input current to the converters.

[4 Marks]
3. The speed of a 120 kw, 1800 rpm, separately excited d.c. motor is controlled by three-phase full converter. The specifications of the converter are 460 V, 280 A. The input to the converter is a three-phase, 415 V, 50 Hz a.c. supply. Neglect the system losses and effect of commutation angle, determine:
 - a) Firing angle of the converter and power factor at rated speed.
 - b) Firing angle and power factor at 10% rated speed.
 - c) Active and reactive power drawn from the system at rated speed.
 - d) Active and reactive power drawn from the system at 10% rated speed.
 - e) Ratio of reactive power drawn at 10% and rated speed.

[10 Marks]

QUESTION FOUR

1. A 6-pole, 50 Hz slip-ring induction motor is controlled by a static Scherbius drive. Determine the angle of firing advance in the inverter at
 - a) 600 rpm
 - b) 800 rpmIf the open circuit standstill slip-ring voltage is 660 V, and the inverter is connected to a 415 V, three-phase system. Neglect overlaps and losses.

[8 Marks]
2. A three-phase, three-wire bidirectional controller supplies a star-connected resistive load of $R = 3 \Omega$ and the line-to-line input voltage is 240 V (RMS) 50 Hz. The firing angle is $\alpha = \frac{\pi}{3}$. Determine:
 - a) The RMS output phase voltage, E_o .
 - b) The input power factor, P_f
 - c) The expression for the instantaneous output voltage of phase 1.

[8 Marks]
3. Discuss two (2) power semiconductor speed control methods of induction motor drives.

[4 Marks]

QUESTION FIVE

1. List at most two (2) classifications of power semiconductor devices and give 2 examples in each classification.

[2 Marks]

2. A three phase to single phase cycloconverter employs six pulse positive and negative group converters. Each converter is supplied from delta/star transformer with per phase turns ratio of 3:1. The supply voltage is 415 V, 60 Hz. The R_L load has $R = 20\Omega$ and at low output frequency, $\omega oL = 5\Omega$. The commutation overlap and thyristor turn-off time limit the firing in the inversion mode to 160° . Determine:

- a) The value of the fundamental RMS output voltage,
- b) The RMS output current,
- c) The output power.

[8 Marks]

4. A two-quadrant chopper operating in the first and fourth quadrant is operated from a 300 V battery. The load is dc motor with $R = 10.1\Omega$, $L = 10\text{ mH}$ and $E_b = 50\text{ V}$, determine:

- a) Duty cycle am for motoring mode
- b) Critical duty cycle for regenerative braking
- c) Duty-cycle to achieve regenerative braking at the rated current of 10 Amp
- d) Power returned to the source during braking
- e) The switching frequency of the devices if the output frequency is 5 kHz.

[10 Marks]