



**MASINDE MULIRO UNIVERSITY OF  
SCIENCE AND TECHNOLOGY  
(MMUST)**

**UNIVERSITY EXAMINATIONS  
2021/2022 ACADEMIC YEAR**

**FOURTH YEAR SECOND SEMESTER MAIN EXAMINATIONS**

**FOR THE DEGREE  
OF  
BACHELOR OF ENGINEERING ELECTRICAL ENGINEERING**

**COURSE CODE:   SPH 441**

**COURSE TITLE:   DIGITAL SYSTEMS DESIGN**

**DATE: MONDAY 25<sup>TH</sup> APRIL, 2022    TIME: 12:00 PM - 2:00 PM**

---

**INSTRUCTIONS TO CANDIDATES**

TIME: 2 Hours

**Answer question ONE and any TWO of the remaining.**

**Symbols used bear the usual meaning.**

MMUST observes ZERO tolerance to examination cheating

This Paper Consists of 4 Printed Pages. Please Turn Over. 

**QUESTION ONE (30 MARKS)**

(a). Distinguish between:

(i) Combinational logic circuits and Sequential circuits.

**(2marks)**

(ii). Synchronous and asynchronous circuits


**(2marks)**

(b) Convert  $9AF_{16}$  to its binary equivalence.

**(3marks)**

(c). The Figure below shows two logic gates connected together. Write a complete VHDL module for the setup.


**(4marks)**

 

(d). List the three levels essential in VHDL description of digital systems

 **(3marks)**

(e). The figure below shows a two input logic gate circuit.



(I). Identify the gate and provide its corresponding logic symbol.

**(2marks)**

(II). Complete the truth table below under the given conditions for the gate in (e) above:

A	B	C (output)
0	0	
1	0	
0	1	
1	1	

(2marks)

(f). Describe the meaning and development of VHDL as a hardware description language

(4marks)

(g). Demorganize the function  $\overline{A.B}$

(3marks)

(h). The XOR gate can be used as a binary to Gray-code converter. Using a clear diagram, illustrate the conversion of  $1010_2$  to its Gray-code equivalent.

(3marks)

(i). Define the following terms:

(I). Real

(1mark)

(II). Time

(1mark)

**QUESTION TWO (20 MARKS)**

(a). List the two factors that need to be declared when using an array in VHDL

(2marks)

(b). Give the VHDL Description of a ROM


(18marks)

**QUESTION THREE (20 MARKS)**

(a). Using IEEE std\_logic, illustrate the VHDL Code for Bi-Directional I/O Pin.

(6marks)

 (b). The Figure below shows a NOR-NOR gate circuit.



Give the corresponding structural VHDL code

(10marks)

(c). Below is a two dimensional array signal, Y:

$$\begin{bmatrix} 5 & 8 \\ 0 & 4 \end{bmatrix}$$

Describe the array in VHDL.

(4marks)

#### QUESTION FOUR (20 MARKS)

(i).

(a). Highlight the concept of Racing in flip-flops.

(5marks)

(b).

(i). How is Racing alleviated.

(2marks)

(ii). Discuss the design a multiplier for two 4-bit positive binary numbers.


(13marks)

#### QUESTION FIVE (20 MARKS)

(a). Describe the construction of an SM chart.

(9marks)

 (b). A 4-to-1 MUX has got four data inputs and two control inputs, A and B as shown below.



The control inputs select which one of the data inputs is transmitted to the output. The logic equation for the 4-to-1 MUX is  $F = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3$ . Use the VHDL statement to model the MUX.

(7marks)

(c). State the VHDL code for the three gates that have the signal A as a common input as given below. Gate 1, 2 and 3 have different delay times of 2ns, 1ns and 3ns respectively.

(4marks)

