



*(University of Choice)*  
**MASINDE MULIRO UNIVERSITY OF  
SCIENCE AND TECHNOLOGY  
(MMUST)**

**MAIN CAMPUS**

**UNIVERSITY EXAMINATIONS  
2021/2022 ACADEMIC YEAR**

**FOURTH YEAR FIRST SEMESTER EXAMINATIONS**

**FOR THE DEGREE  
OF  
BACHELOR OF SCIENCE IN MECHANICAL AND INDUSTRIAL ENGINEERING**

**COURSE CODE: MIE 451**

**COURSE TITLE: INDUSTRIAL MEASUREMENTS AND INSTRUMENTATION**

**DATE: Tuesday, April 19<sup>th</sup>, 2022**

**TIME: 3.00- 5.00 PM**

---

**INSTRUCTIONS TO CANDIDATES**

Question ONE (1) is compulsory  
Answer Any Other THREE (3) questions

TIME: 3 Hours

**MMUST observes ZERO tolerance to examination cheating**

*This Paper Consists of 4 Printed Pages. Please Turn Over.*

▶

Question 1 is compulsory.

1. (a) State any two advantages of electronic measurement. (2mks)
  - (b) State and explain static and dynamic characteristics of Instruments (4mks)
  - (c) Using a block diagram, describe a generalized measurement system and the functions of each element. (3mks)
  - (d) Explain 3 sources of errors in instruments (3 mks).
  - (e) In a test on a Bakelite sample at 20 kV, 50 Hz by a Schering Bridge, having a standard capacitor of 106 pF, balance was obtained with a capacitance of  $0.35 \mu\text{F}$  in parallel with a non-inductive resistance of  $318 \Omega$ , the non-inductive resistance in the remaining arm of the bridge being  $130 \Omega$ . Determine
    - (i) Capacitance (3mks)
    - (ii) Power factor (3mks)
    - (iii) Equivalent series resistance. (3mks)
  - (f) With the aid of a neat and well labelled diagram of a Maxwell Wien Bridge, derive the expression of how an inductance of an unknown value could be calibrated. (7mks)
  - (g) Define a wave analyzer. (2mks)
- 
2. (a) What is a Transducer? (1mk)
  - (b) (i) Explain various classifications of transducers. (2 mks).
  - (ii) State the key requirements of good transducers. (2 mks).
  - (iii) Why is mercury-in-glass not preferred in measuring temperature? (2mks)
  - (c) A thermocouple circuit uses Chrome- Alumel thermocouple which gives an emf of  $35\text{mV}$  when measuring a temperature of  $800^\circ\text{C}$  with reference temperature of  $0^\circ\text{C}$ . The resistance of the meter coil  $R_m$  is  $50 \Omega$  and a current of  $0.1 \text{ mA}$  gives full scale deflection. The resistance of junction and leads,  $R_e$  is  $12 \Omega$ . Calculate.
    - (i) The resistance of the series resistance if a temperature of  $800^\circ\text{C}$  is to give full deflection. (2 mks)
    - (ii) The approximate error due to rise of  $1.25 \Omega$  in  $R_e$ . (2mks)

- (iii) The approximate error due to rise of  $10^{\circ}$  C in the copper coil of the meter. The resistance temperature coefficient of the coil is  $0.0045/^{\circ}$  C. (2mks)
- (d) What are thermopiles and where are they used? (2 mks)
- (e) With the help of diagrams, describe the working principle and application of a linear Variable Differential Transformer (5 mks).
3. (a) With the help of a block diagram, describe the building block of a digital instrument. (3mks)
- (b) Using a clearly labelled block diagram of a basic digital multimeter, describe how current and resistance are measured. (6 mks).
- (c) Using a block diagram of microprocessor based instrument, explain how impedance measurement can be obtained. (6 mks).
- (d) A barium titanate pickup has the dimensions of 5 mm by 5 mm by 1.25 mm. The force acting on it is 5N. The charge sensitivity of barium titanate is 150 pC/N and its permittivity is  $12.5 \times 10^{-9}$  F/m. If the modulus of elasticity of barium titanate is  $12 \times 10^6$  N/m<sup>2</sup>. Calculate the strain, the charge and capacitance of the crystal. (5mks).
4. (a) Draw Wheatstone's bridge and describe how it is used to measure resistance under balanced conditions. (5mks).
- (b) With reference to (a) above, given that R1 and R2 have a common point with the switch and connected to positive terminal of DC supply while R3 and Rx have a common point with the neutral of the DC supply. Calculate Rx where R1=10k $\Omega$ , R2=15k $\Omega$  and R3=40k $\Omega$ . (3mks)
- (c) State the limitations of Wheatstone's bridge (3mks).
- (d) A Maxwell Bridge is used to measure the inductive impedance. The bridge constants at balance are: C1= 0.01  $\mu$ F, R1=470 k $\Omega$ , R2=5.1 k $\Omega$ , R3=100 k $\Omega$ . Find the series equivalent of the unknown impedance. (5mks).
- (e) An ac bridge has the following constants. (Refer to Fig 1).  
 Arm AB – capacitor of 0.5  $\mu$ F in parallel with 1 k $\Omega$  resistance.  
 Arm AD- resistance of 2 k $\Omega$ .

Arm BC- capacitor of  $0.5 \mu\text{F}$ .

Arm CD- Unknown capacitor  $C_x$  and  $R_x$  in series.

Frequency - 1 kHz.

Determine the unknown capacitance and dissipation factor. (4 mks)

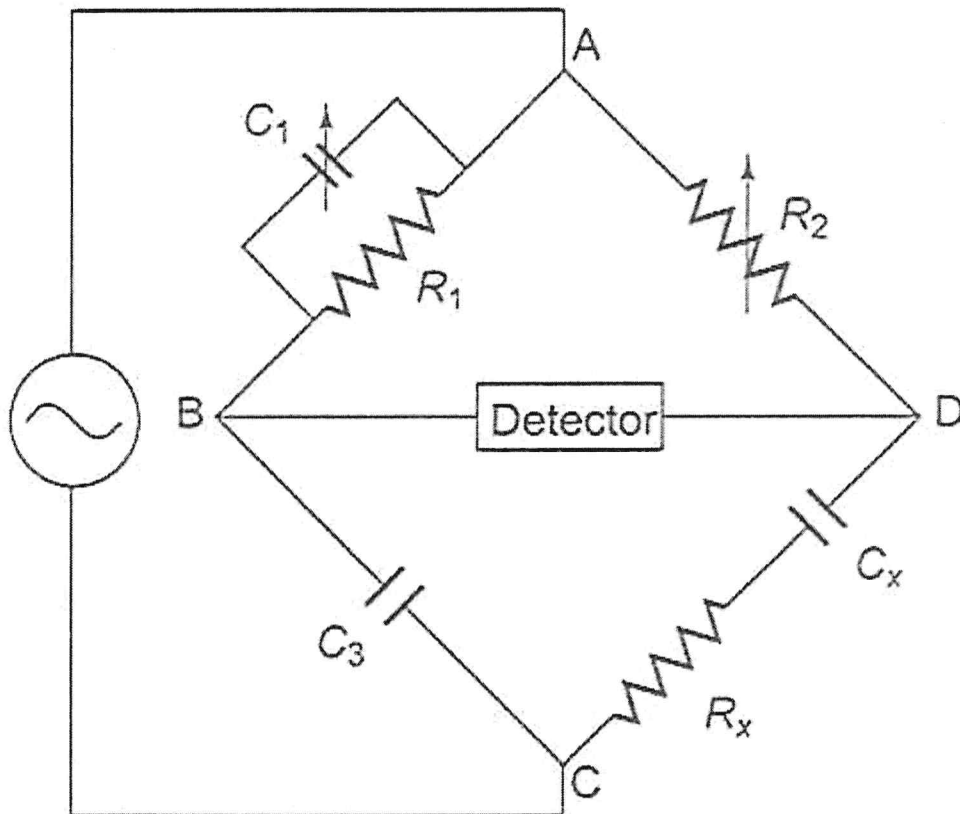


Fig 1.

5. (a) List the major components of a CRT. (2 mks).
- (b) Draw the basic block diagram of an Oscilloscope and state the functions of each element. (6mks).
- (c) List the advantages of using negative voltage in a CRO. (2mks).
- (d) Describe with the help of a diagram the operation of Dual Trace Oscilloscope. (5 mks).
- (e) State and explain the general classifications of digital displays. (5mks)