



(University of Choice)  
**MASINDE MULIRO UNIVERSITY OF  
SCIENCE AND TECHNOLOGY  
(MMUST)**

**MAIN CAMPUS**

**UNIVERSITY EXAMINATIONS  
2021/2022 ACADEMIC YEAR**

**THIRD YEAR SECOND SEMESTER MAIN EXAMINATIONS**

**FOR THE DEGREE  
OF  
BACHELOR OF SCIENCE IN ELECTRICAL AND COMMUNICATIONS  
ENGINEERING**

**COURSE CODE: ECE 326**

**COURSE TITLE: ANALOGUE ELECTRONICS II**

**DATE: MONDAY, APRIL, 25<sup>TH</sup>, 2022**

**TIME: 12:00 – 2:00 PM**

---

**INSTRUCTIONS TO CANDIDATES**

Question ONE (1) is compulsory  
Answer Any Other TWO (2) questions

TIME: 2 Hours


**MMUST observes ZERO tolerance to examination cheating**

This Paper Consists of 6 Printed Pages. Please Turn Over.




**Question One (30mks)**

- (a) i) Define the following terms: (4mks)
- i) Virtual ground
  - ii) Output offset voltage
  - iii) Common-Mode Rejection Ratio
  - iv) Slew rate
- ii) Derive the equation for closed loop gain for the non-inverting amplifier. (3mks)
- (b) For the circuit shown in Figure 1 below, find the output voltage if the input voltage is  $0.4 \sin(1000t)$  V and sketch the output waveform (4mks)
- The values of capacitance and resistance are:  $C = 10\mu\text{F}$ ,  $R = 3\text{k}\Omega$

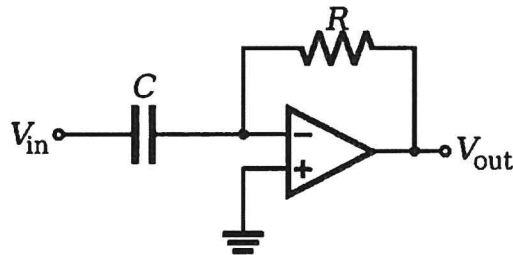


**Figure 1**

- (c) The Figure 2 shows a difference amplifier. (6mks)
- i) Derive the equation for the output voltage ( $V_o$ ).
  - ii) Given that  $\frac{R_f}{R_1} = \frac{R_g}{R_2}$  where  $R_2 = 2\text{k}\Omega$ ;  $R_g = 4\text{k}\Omega$ ; , and inputs  $V_1 = 0.5\text{V}$  and  $V_2 = 0.75\text{V}$ , compute  $V_o$ .

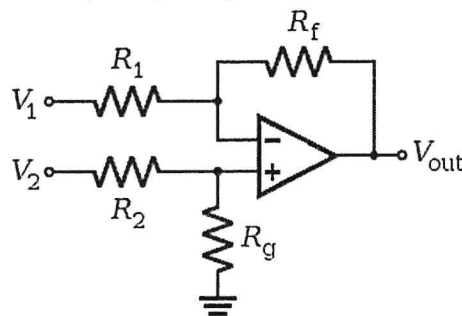

**Figure 2**

- (d) With the aid of a circuit diagram and graphical illustration of input- output waveforms, describe the operation of a monostable Op-Amp multivibrator circuit. (8mks)
- (e) Considering the circuit in Figure 3, show that the output voltage is proportional to the natural logarithm of the input voltage  $V_{in}$  for a fixed value of resistance  $R_1$ . (5mks)

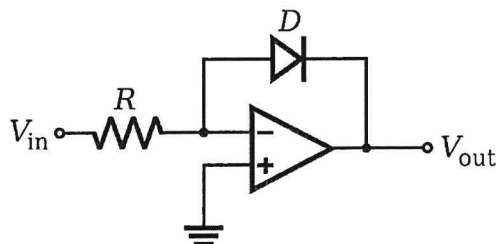


**Figure 3**

**Question Two (20mks)**

- (a) Show that the output of an integrator in Figure 4 is given by;


(6mks)

$$V_o = -\frac{1}{RC} \int_0^t V_i dt$$

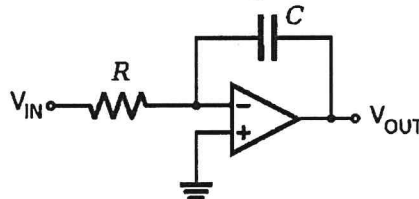


**Figure 4**

- (b) With the aid of a circuit diagram, explain how half-wave precision rectifiers can be used to clip extremely low-level input signals (6mks)
- (c) For the Astable multivibrator circuit shown in Figure 5, calculate the frequency of oscillation. Sketch the input-output waveforms at supply rail of  $\pm 5V$ . (4mks)

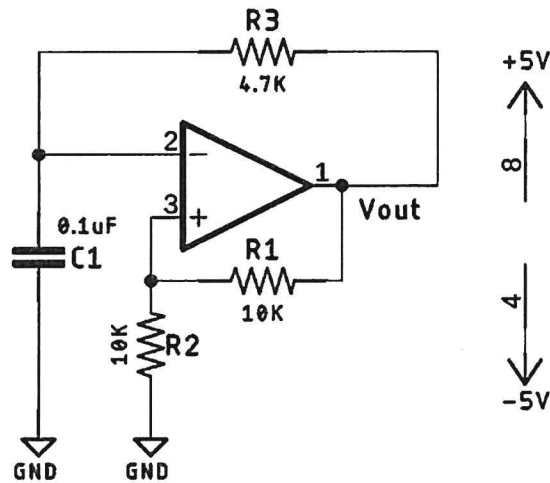

**Figure 5**


- (d) For the circuit of Figure 6, Op-amp slew rate is  $SR = 0.5V/\mu s$ ;  $R_f = 240k\Omega$ ;  $R_{in} = 10k\Omega$ ;  $V_{in} = 0.02V$ ,  $\omega = 300 \times 10^3 rad/s$ , determine the maximum operating frequency and from the result, comment whether distortion occurs. (4mks)

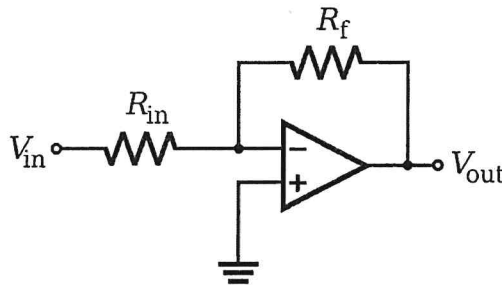

**Figure 6**


**Question Three (20mks)**

- (a) The circuit diagram in Figure 7 is subjected to a square wave input of  $\pm 5V$  at 1kHz frequency that changes in  $0.2ms$ . This supply voltage is  $V_{cc} = \pm 12V$ . Determine the output voltage if  $C = 0.01\mu F$ ,  $R = 15k\Omega$  and sketch the output waveform.

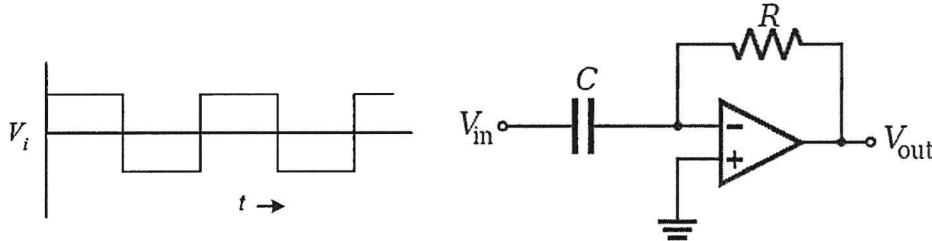


**Figure 7**

- (b) The Op-Amp circuit in Figure 8 has the following information on the data sheet:  $Z_{in} = 2 M\Omega$ ,  $Z_{out} = 75 \Omega$ , and  $A_{ol} = 200,000$ . If the feedback resistors are  $R_1 = 10k\Omega$ ,  $R_2 = 230k\Omega$ , determine;
- The input and output impedances due to negative feedback
  - The closed-loop voltage gain
  - If the Op-Amp is used in the voltage-follower configuration determine the input and output impedances.

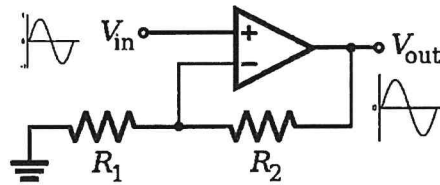

**Figure 8**

- (c) The circuit in Figure 9 shows an inverting amplifier with a supply voltage of  $750mV$  at the inverting input terminal and  $V_{cc} = \pm 10V$
- Find the output voltage if the variable resistor  $R_x = 8k\Omega$
  - Determine the maximum value of  $R_x$  for the Op-Amp to avoid saturation.

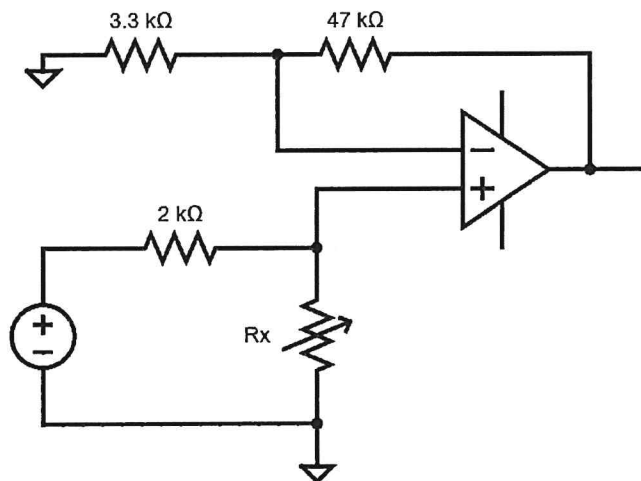

**Figure 9**

**Question 4 (20mks)**

Calculate;

- i) The rate of change of the output voltage during the capacitor's charging time.
- ii) The total change in voltage.
- iii) Draw the output waveform.

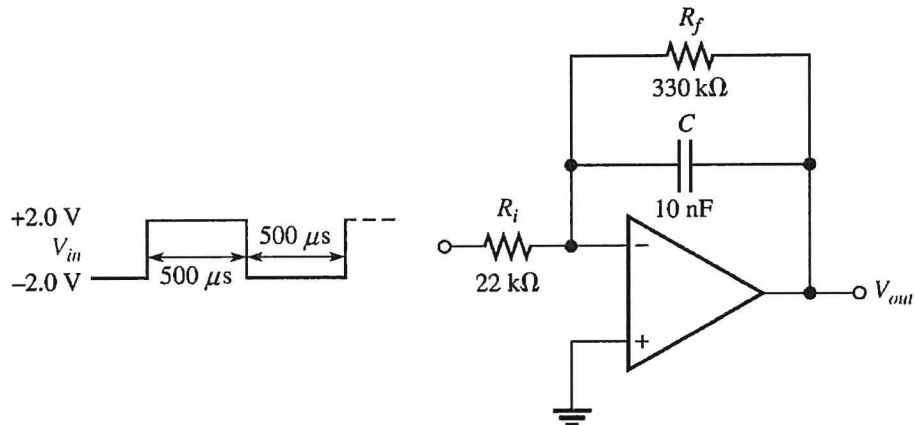


Figure 10

- (b) Design an Op-Amp circuit with inputs  $V_1$  and  $V_2$  such that; (7mks)

$$V_o = 7.5V_1 - 2V_2$$

- (c) For the instrumentation amplifier circuit shown in the Figure 11 assuming that no current flows into the Op-Amps, and neglecting the input offset voltage, the same voltage  $V_{in}$  is seen at both inputs  $V_+$  and  $V_-$ . Determine the load current  $I_L$ .

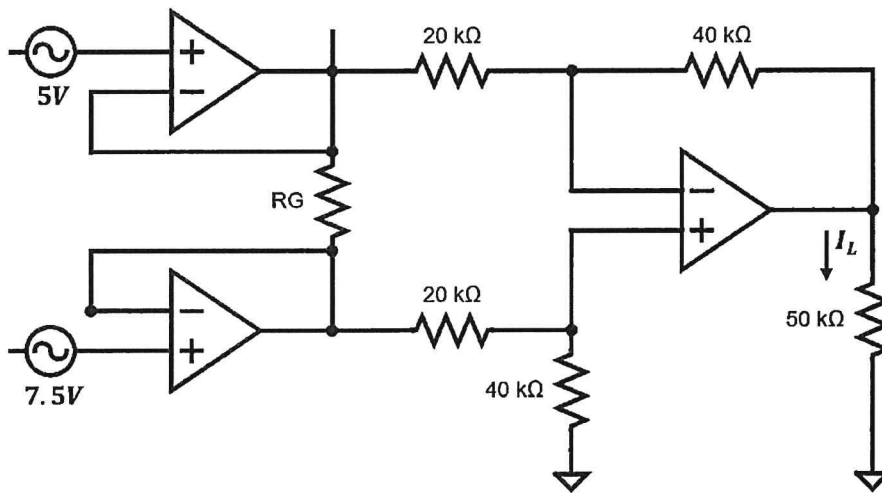
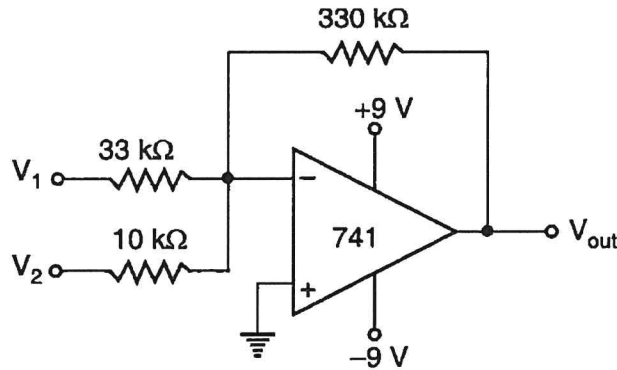


Figure 11

**Question 5 (20mks)**

- (a) Calculate the output voltage for the circuit of Figure 12, for the following (3mks)  
inputs;  $V_1 = 50 \sin(1000t) \text{ mV}$ ;  $V_2 = 10 \sin(3000t) \text{ mV}$

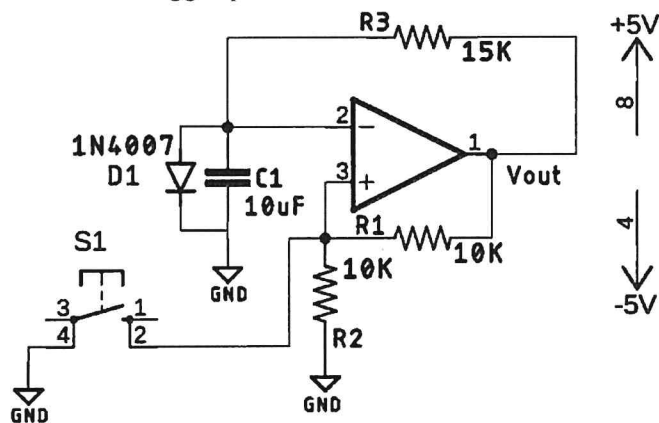


**Figure 12**

- (b) An Op-Amp monostable circuit is constructed using the components as shown (8mks)  
in Figure 13. If it is supplied from a  $\pm 5V$  and the timing period is initiated with  
a  $10\text{ms}$  pulse.


Calculate:

- The circuit's timing period ( $\tau$ )
- Capacitor recovery time
- Total time between trigger pulses



**Figure 13**

- (c) For the circuit of Figure 13 determine the value of resistor  $R_x$  so that the output (9mks)  
voltage is zero.

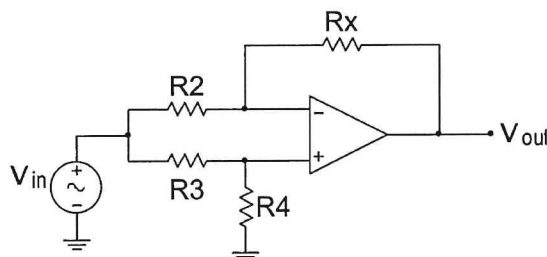

**Figure 13**