



(University of Choice)
**MASINDE MULIRO UNIVERSITY OF
SCIENCE AND TECHNOLOGY
(MMUST)**

MAIN CAMPUS

**UNIVERSITY EXAMINATIONS
2021/2022 ACADEMIC YEAR**

**FOURTH YEAR FIRST SEMESTER SPECIAL/SUPPLEMENTARY
EXAMINATIONS**

**FOR THE DEGREE
OF
BACHELOR OF SCIENCE IN ELECTRICAL AND COMMUNICATIONS
ENGINEERING**

COURSE CODE: ECE 413

COURSE TITLE: INSTRUMENTATION

DATE: Monday, 3rd October, 2022 TIME: 3-5pm

INSTRUCTIONS TO CANDIDATES

Question ONE (1) is compulsory
Answer Any Other TWO (2) questions

TIME: 2 Hours

MMUST observes ZERO tolerance to examination cheating

This Paper Consists of 4 Printed Pages. Please Turn Over.



Question 1 (30mks)

- (a) i) State three characteristics of instrumentation amplifiers [3mks]
ii) With regards to signal conditioning, define the following terms: [4mks]
i) Multiplexing:
ii) Quantization
iii) Quantization error
iv) Resolution of an Analogue-to-Digital Converter:
- (b) i) State the principle of operation of piezoelectric sensors and [6mks]
explain the working of piezo-electric accelerometers with the aid
of a well labelled diagram.
ii) Show that the output voltage (V) of a piezoelectric crystal is [2mks]
proportional to applied pressure P .
- (c) With the aid of a block diagram, describe the internal structure of a [6mks]
smart sensor.
- (d) The level of Hydrogen peroxide ($\rho = 1450 \text{ kg/m}^3$) in a cylindrical [4mks]
vessel with a diameter of 2.5m and weight $w = 100 \text{ kg}$, can vary
from 0 to 3m . The minimum variation in level that can be detected
is 10cm . Design 4 load cells that can be used to measure the
variations in height. [Take $g = 9.8\text{N/kg}$]
- (e) With the aid of a diagram, describe the working of a ramp ADC [5mks]
converter.

Question 2 (20mks)

- (a) i) State the working principle of pyroelectric sensor and explain [5mks]
using a sketch how it behaves as a *charge generator* when
subjected to incident infrared radiation.
ii) Describe the application of pyroelectric sensors in detecting [5mks]
human motion.
- (b) i) An NTC thermistor made of chromium has a resistance of $1\text{k}\Omega$ [4mks]
at $T = 100^\circ\text{C}$, and $100\text{k}\Omega$ at 0°C . Calculate the resistance at
 $T = 40^\circ\text{C}$.
ii) The thermistor (R_0) is connected into a bridge circuit and [3mks]
supplied with 15V as shown in Figure 1. At balanced condition,
 $R_0 = R_a = R_b = R_c = 100\text{k}\Omega$. At $T = 40^\circ\text{C}$, calculate the voltage that
the thermistor must resolve to define 1°C change in temperature.

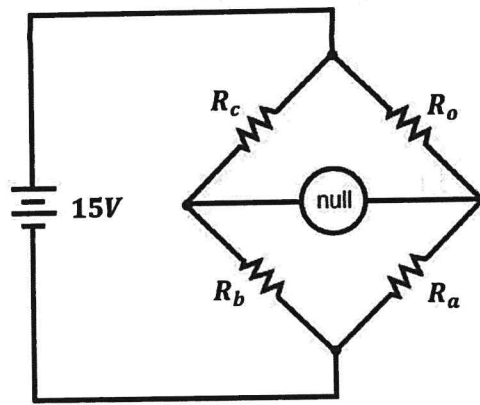


Figure 1

- iii) The differential output voltage from the bridge circuit contains high frequency signals and therefore it's fed into the input of the instrumentation amplifier circuit as shown in Figure 2. If $R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = 33\text{ k}\Omega$, determine R_G so that the corresponding output $V_o = 10\text{V}$. [3mks]

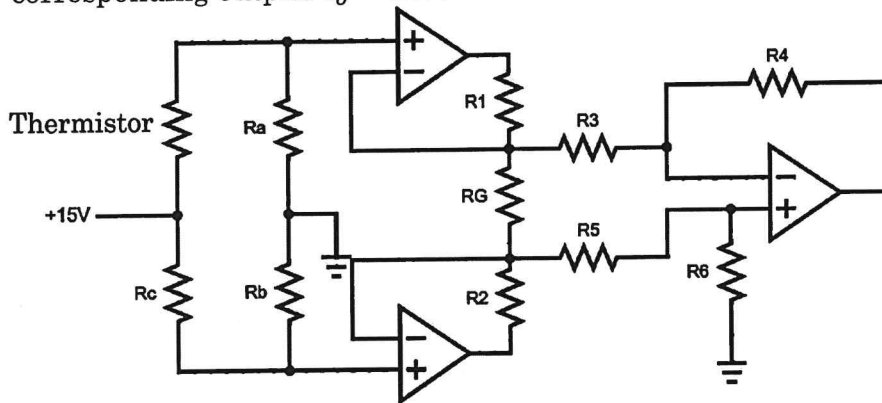


Figure 2

Question 3 (20mks)

- (a) Explain the working principle of magnetoresistive effect and give two applications. [5mks]
- (b) i) A 2.5 mm thick quartz piezoelectric crystal having a voltage sensitivity of 0.055Vm/N is subjected to a pressure of 1.4MN/m^2 . If the permittivity of quartz is $40.6 \times 10^{-12}\text{F/m}$, Calculate; [4mks]
 i) The output voltage
 ii) Charge sensitivity
- ii) If the output voltage from the sensor is fed through a charge amplifier, into a ramp A/D converter with a 16-bit precision and a maximum quantization error of $\pm 0.05125\text{V}$. Assuming uniform quantization error, calculate: [3mks]
 i) The quantization interval
 ii) Range of possible input signals if the minimum input is 0V .
- (c) State five advantages of intelligent instruments over dumb instruments. [5mks]
- (d) A $10\text{k}\Omega$ NTC thermistor has a β value of 3455 between the [3mks]

temperature range of 25°C and 100°C. Calculate its resistive value at 25°C and at 100°C.

Question 4 (20mks)

- (a) With the aid of a well labelled circuit diagram, describe how a LVDT transducer can be used with a bellows to measure changes in pressure levels. [8mks]
- (b) Highlight five functions performed by data acquisition software. [5mks]
- (c) A potentiometer has a total resistance of 15.5kΩ over the entire length of 24cm. It is excited by 10V DC. The output voltage is measured by an analogue voltmeter with an input resistance $R_L = 35k\Omega$, connected as load of the potentiometer. If the wiper is at 16cm, calculate: [8mks]
 - i) the output voltage indicated by the analogue voltmeter
 - ii) the non-linearity error introduced by the analogue voltmeter and compare with the error caused if a digital voltmeter with $R_L = 12M\Omega$ was used.

Question 5 (20mks)

- (a) Using well labelled circuit diagrams, explain the working of voltage-to-frequency converters. [7mks]
- (b) A platinum resistance temperature detector (RTD) is connected as shown in the Figure 3. The buffer A1 decouples the voltage divider from the inverting Op-Amp. The parameters of the RTD are; $\alpha = 0.01/^\circ\text{C}$, $T_0 = 0^\circ\text{C}$, $R_0 = 100k\Omega$. The circuit parameters are $V_s = 5V$, $R_1 = 3R_0$, $V_{out} = \pm 10V$. Calculate the measurable interval of temperature when V_{out} changes from 0V to -10V. [4mks]

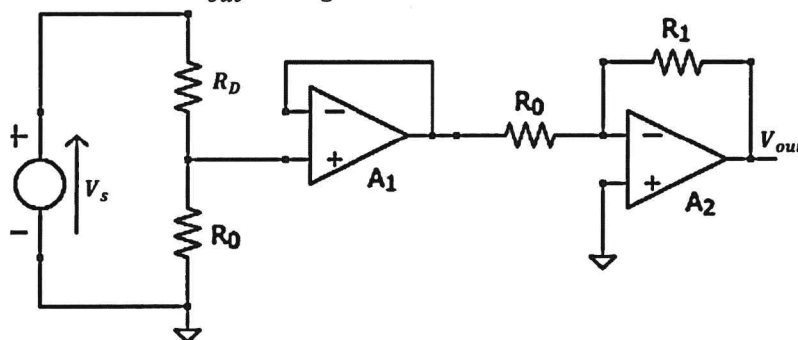


Figure 3

- (c) i) Explain by use of a well labelled diagram how a capacitive accelerometer can be used for triggering airbags in automobiles. [3mks]
- ii) A capacitance transducer has two plates of area 500mm^2 , separated by a distance of 0.2mm. A linear displacement reduces the gap to 0.18mm. If the dielectric is air having a permittivity of $8.85 \times 10^{-12} \text{F/m}$. Calculate; [3mks]
 - i) the change in capacitance.
 - ii) the sensitivity of the capacitive transducer [3mks]