



(University of Choice)

**MASINDE MULIRO UNIVERSITY OF
SCIENCE AND TECHNOLOGY
(MMUST)**

MAIN CAMPUS

**UNIVERSITY EXAMINATIONS
2022/2023 ACADEMIC YEAR**

FOURTH YEAR FIRST SEMESTER EXAMINATIONS

**FOR THE DEGREE
OF
BACHELOR OF SCIENCE IN MECHANICAL AND
INDUSTRIAL ENGINEERING**

COURSE CODE: ECE 413

COURSE TITLE: INSTRUMENTATION

DATE: 20TH DECEMBER, 2022 TIME: 12: 00 PM – 2:00 PM

INSTRUCTIONS TO CANDIDATES

ANSWER QUESTION ONE AND ANY OTHER TWO QUESTIONS.
QUESTION ONE CARRIES 30 MARKS AND ALL OTHERS 20 MARKS EACH.

TIME: 2 Hours

MMUST observes ZERO tolerance to examination cheating

This Paper Consists of 4 Printed Pages. Please Turn Over. 

Question One (30mks)

- (a) i) State and explain the working principle of the following sensors: [5mks]
- i) Load cell
 - ii) Polyvinylidene Fluoride tactile sensor
 - iii) Thermocouple
 - iv) Hall sensor
 - v) Pyroelectric infrared sensor
- ii) Highlight five advantages of intelligent instruments over dumb instruments. [5mks]
- (b) Describe with the aid of a circuit diagram and waveforms how an analogue output voltage from a sensor can be sampled and held before conversion to digital signal. [5mks]
- (c) A linear potentiometric displacement sensor in Fig.1 has a maximum resistance of R_p and a range of 0 to 20mm. If the sensor is supplied with a voltage V_s and connected to a digital voltmeter of input resistance R_L at terminals A and B. Determine the ratio of the output to input voltage as a function of the fractional potentiometric resistance x . [5mks]

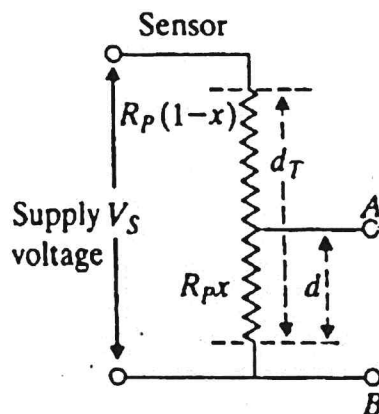


Fig.1

- (d) Outline four tasks that can be performed by LabVIEW graphical programming environment. [4mks]
- (e) Describe the working of a digital Ramp ADC using a well labelled diagram. [6mks]

Question Two (20mks)

- (a) A potentiometer has a total resistance of $12\text{k}\Omega$ over the entire length of 24cm . The output voltage is measured by a digital voltmeter with $R = 12\text{M}\Omega$ connected across the output terminals. If it is supplied by 12V DC and the wiper is at 18cm , calculate: [6mks]
- the output voltage
 - the non-linearity error introduced by the digital voltmeter
- (b) If the analogue voltage from potentiometer is to be fed into a 4-bit successive approximation ADC, through some intermediate circuitry. [9mks]
- describe how a digital equivalent signal is generated from the value obtained in (a) (i) above.
 - Draw the circuit used for conversion
- (c) Strain in a cantilever beam is monitored using a strain gauge of resistance $1\text{k}\Omega$, $GF = 2$ and temperature Coefficient of resistance of $10^{-5}/^\circ\text{C}$ at room temperature, connected into bridge circuit. At maximum beam deformation, the strain is 4.5 . [5mks]
- Calculate the change in resistance of the gauge if it is strained 0.1%
 - Calculate the change in effective strain when the room temperature increases by 10°C ;
 - Suggest a way of reducing this temperature effect.

Question Three (20mks)

- (a) i) Explain the working principle of negative temperature coefficient (NTC) thermistor. [5mks]
- ii) An NTC thermistor made of chromium has a resistance of $1k\Omega$ at $T = 100^\circ\text{C}$ and $100k\Omega$ at 0°C . Calculate the resistance at $T = 45^\circ\text{C}$.
- (b) If the Chromium thermistor (R_0) is connected into a bridge circuit and supplied with $15V$ as shown in Fig. 2. Calculate the voltage that the thermistor must resolve to define 1°C change in temperature. Consider a balanced condition $R_0 = R_a = R_b = R_c = 100k\Omega$ and temperature changes from 0 to 45°C . [4mks]

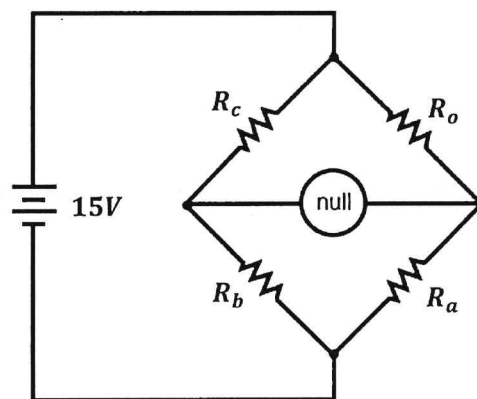


Fig. 2

- (c) The differential output voltage from the bridge circuit contains high frequency signals and therefore it's fed into the input of the instrumentation amplifier circuit as shown in Fig. 3. If $R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = 33k\Omega$, determine the gain resistance R_G that gives $V_o = 7V$. [4mks]

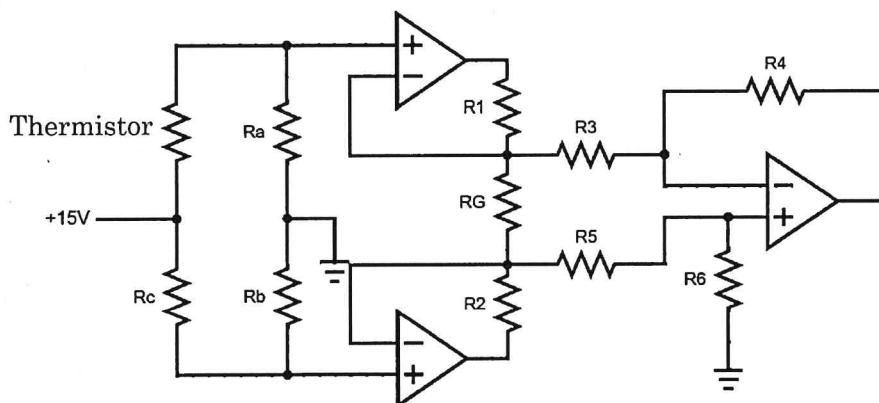


Fig. 3

- (d) The $7V$ analogue output from the instrumentation amplifier in (b) is to be converted to a digital word. A 3-bit Flash ADC is to be used. Describe using a circuit diagram how the digital conversion occurs. [7mks]

Question 4 (20mks)

- (a) The data in the table gives the strain values against differential pressure for a strain gauge bonded to bellows. Pressure ranges from 120kPa to 210kPa. [4mks]

Pressure (kPa)	120	150.3	177.5	210
Strain (μm)	70	85	100	115

Assuming a linear relationship between the minimum and maximum values, determine the non-linearity error as a percentage of full range input at $\varepsilon = 100\mu\text{m}$.

- (b) With aid of a well labelled diagram, describe the structure of a force sensitive resistor, explain the working principle and give TWO applications. [6mks]
- (c) Using well labelled circuit diagrams, explain how voltage-to-frequency converters generate a frequency signal. [5mks]
- (d) Describe the working of a variable reluctance tachogenerator. [5mks]

Question 5 (20mks)

- (a) With the aid of a well labelled circuit diagram, describe how an LVDT transducer can be used with a bellows to measure changes in fluid pressure levels. [5mks]
- (b) An LVDT with a range of $\pm 10\text{mm}$ is connected to a 15V voltmeter through an amplifier of gain 250. The voltmeter scale has 100 divisions and can be read up to $1/5^{\text{th}}$ of a division. A 0.4mm core displacement produces a differential output of 2mV. Calculate: [5mks]
- The sensitivity of the LVDT at the amplified output
 - The output resolution of the instrument
 - Number of bits required for an ADC when its output is to be digitized
- (b) Four Piezoelectric crystals of charge sensitivity $2\text{Pc}/\text{N}$, area = 1cm^2 , 0.1 cm thickness and $\varepsilon_r = 5$. They are arranged in parallel, and are subjected to a force of 24N. [10mks]
- Take $\varepsilon_0 = 8.85 \times 10^{-12}\text{F/m}$; $E = 9 \times 10^{10}\text{Pa}$
- Determine:
- the voltage across the electrodes for each crystal
 - the change in crystal thickness
 - If the output voltage from the sensor is fed through a charge amplifier, into a 16-bit ramp A/D converter with 1.5V resolution. Assuming uniform quantization error of $\pm 0.05125\text{V}$, calculate the range of possible input signals.

