



**MASINDE MULIRO UNIVERSITY OF
SCIENCE AND TECHNOLOGY
(MMUST)
MAIN CAMPUS**

**UNIVERSITY EXAMINATIONS
2022/2023 ACADEMIC YEAR**

**SECOND YEAR FIRST SEMESTER EXAMINATIONS
FOR THE DEGREE
OF
BACHELOR OF SCIENCE IN COMPUTER SCIENCE**

COURSE CODE: BCS 211

COURSE TITLE: DIGITAL ELECTRONICS

DATE: 05/12/2022

TIME: 08:00-10:00AM

INSTRUCTIONS TO CANDIDATES

- Answer Questions ONE and ANY OTHER TWO.

TIME: 2 Hours

QUESTION ONE 30 MARKS (COMPULSORY)

- a. Find the hex sum of $(93)_{16} + (DE)_{16}$. 4 Marks
- b. Perform 2's complement subtraction of $(7)_{10} - (11)_{10}$. 3 Marks
- c. Evaluate $x = \overline{A}.B + C(\overline{A.D})$ using the convention A = True and B = False. 4 Marks
- d. Simplify the Boolean expression $F = C(B + C)(A + B + C)$. 6 Marks
- e. Simplify the following expression into sum of products using Karnaugh map
 $F(A,B,C,D) = \sum(1,3,4,5,6,7,9,12,13)$ 6 Marks
- f. Draw the circuit diagram of a Master-slave J-K flip-flop using NAND gates. What is race around condition? How is it eliminated in a Master-slave J-K flip-flop? 7 Marks

QUESTION TWO 20 MARKS

- a. Determine the binary numbers represented by the following decimal numbers.
(i) 25.5 (ii) 10.625 (iii) 0.6875 6 Marks
- b. Simplify the given expression to its Sum of Products (SOP) form. Draw the logic circuit for the simplified SOP function $Y = (A + B)(A + \overline{AB})C + \overline{A}(B + \overline{C}) + \overline{AB} + ABC$ (5)
- c. Prove the following Boolean identities.
(i) $XY + \overline{YZ} + \overline{Y}Z = XY + Z$
(ii) $A.B + \overline{A}.B + \overline{A}.\overline{B} = \overline{A} + B$ 4 Marks
- d. Prove the following equations using the Boolean algebraic theorems:
(i) $A + \overline{A}.B + A.\overline{B} = A + B$ (ii) $\overline{A}BC + A\overline{B}C + AB\overline{C} + ABC = AB + BC + AC$ 5 Marks

QUESTION THREE 20 MARKS

- a. A combinational circuit has 3 inputs A, B, C and output F. F is true for following input combinations
A is False, B is True
A is False, C is True
A, B, C are False
A, B, C are True
- (i) Write the Truth table for F. Use the convention True=1 and False = 0.
(ii) Write the simplified expression for F in SOP form.
(iii) Write the simplified expression for F in POS form.
(iv) Draw logic circuit using minimum number of 2-input NAND gates. 6 Marks

b.

Prove the following Boolean identities using the laws of Boolean algebra:

(i) $(A + B)(A + C) = A + BC$

(ii) $ABC + A\bar{B}C + AB\bar{C} = A(B + C)$

4 Marks

c. The Karnaugh map for a SOP function is given below in Fig.1. Determine the simplified SOP Boolean expression. 5 Marks

		CD →			
		00	01	11	10
AB ↓	00	1	1		1
	01		1		
	11				
	10	1	1		1

Fig.1


d.

e. What are universal gates? Construct a logic circuit using NAND gates only for the expression $x = A.(B + C)$. 5 Marks

QUESTION FOUR 20 MARKS

a. What is a half-adder? Explain a half-adder with the help of truth-table and logic diagram. 5 Marks

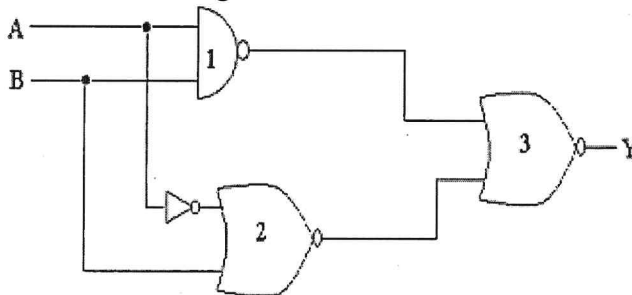b. Find the Boolean expression for the logic circuit shown below. 3 Marks



c.

d. With relevant logic diagram and truth table explain the working of a two input EX-OR gate. 6 Marks

e. With the help of clocked JK flip flops and waveforms, explain the working of a three bit binary ripple counter. Write truth table for clock transitions. 6 Marks

QUESTION FIVE 20 MARKS

a. Distinguish between ROM, PROM, EPROM, EEPROM 6 Marks

b. State and prove Demorgan's laws. 4 Marks

c. Simplify the expressions using Boolean postulates 6 Marks

(i) $XY + XYZ + X(Y + XY)$

(ii) $Y = (A + B)(A + C)(B + C)$

(iii) $XY + XZ + XYZ(XY + Z)$

d. Write the expression for Boolean function $F(A, B, C) = \sum m(1,4,5,6,7)$ in standard POS form. 4 Marks