



(University of Choice)

**MASINDE MULIRO UNIVERSITY OF
SCIENCE AND TECHNOLOGY
(MMUST)**

MAIN CAMPUS

**UNIVERSITY EXAMINATIONS
2022/2023 ACADEMIC YEAR**

THIRD YEAR SECOND SEMESTER EXAMINATIONS

**FOR THE DIPLOMA
IN
ELECTRICAL AND ELECTRONICS ENGINEERING**

COURSE CODE: DEE 077

COURSE TITLE: DIGITAL ELECTRONICS

DATE: Wednesday 19th April, 2023

TIME: 9.00 a.m – 11.00 a.m

INSTRUCTIONS TO CANDIDATES

ANSWER QUESTION ONE AND ANY OTHER TWO QUESTIONS.
QUESTION ONE CARRIES 30 MARKS AND ALL OTHERS 20 MARKS EACH.


TIME: 2 Hours

MMUST observes ZERO tolerance to examination cheating

This Paper Consists of 4 Printed Pages. Please Turn Over. 

QUESTION ONE (30mks)

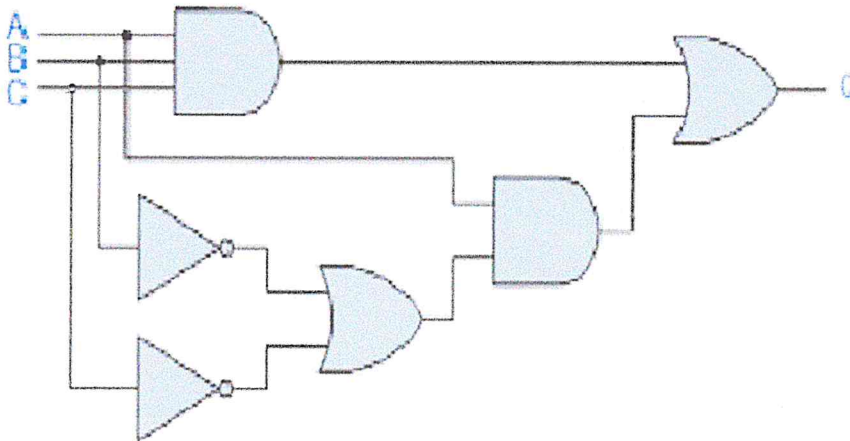- a) State two advantages and two disadvantages of digital representation (4mks)
- b) Convert the following Decimal into the equivalent binary (6mks)
 - i) 85_{10}
 - ii) 29_{10}
 - iii) 40_{10}
- c) Convert the following into Binary Coded Decimal (BCD) (4mks)
 - i) 8579_{10}
 - ii) 100_{10}
- d) Name four applications of flip flops (4mks)
- e) A seven-bit hamming code received at the receiver is 1100100. Is there an error in the received code? If yes what is the correct code? (4mks)
- f) Derive the output of the logic circuit below in terms of the inputs (6mks)



QUESTION TWO (20mks)

- a) Simplify using K-map the Boolean expression below (6mks)
$$F = ABC + \bar{A} \bar{B} \bar{C} + \bar{A} \bar{C} D$$
- b) Draw the logic circuit for the simplified expression in (a) above (4mks)
- c) With the aid of truth table and symbols explain the two special gates (6mks)
- d) Draw the logic circuit that performs the following function ;

An alarm comes on when door is closed and the level of liquid in tank X is equal to that in tank Y (4mks)

QUESTION THREE (20mks)

- a) Outline 3 application areas of number system (6mks)
- b) Using K map simplify the following Boolean expression and implement it using logic circuits


$$F(W, X, Y, Z) = \sum (3,5,7, 8, 9) + \sum \Phi (0, 1, 2, 10, 11, 14,15) \quad (14mks)$$

QUESTION FOUR (20mks)

- a) Differentiate between the combinational logic circuits and sequential logic circuits. (2mks)
- b) Convert $F_{3_{16}}$ to Octal number system. (2mks)
- c) State three application of the Boolean Algebra (3mks)
- d) A company has 4 directors ABC and D, the percentage shares hold by them are 35,30,25,10 respectively. Their voting power is proportional to shares held by them. Any major decision must have a support of 60% of share as stock. Design combinational logic circuit for voting in the company (13mks)

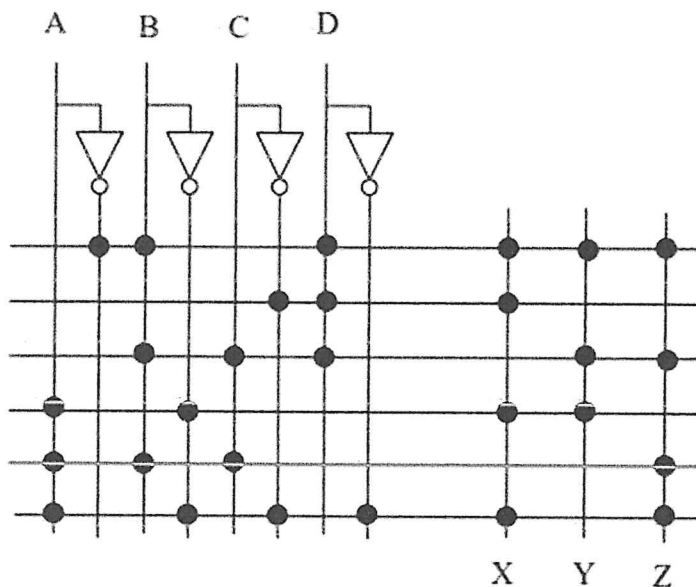QUESTION FIVE (20mks)

The internal connection diagram for a PLA is given below.



(a) Write the equations realized by the PLA. (6mks)

(b) Specify the truth table for a ROM which would realize the same function (14mks)