



(University of Choice)

**MASINDE MULIRO UNIVERSITY OF
SCIENCE AND TECHNOLOGY
(MMUST)**

MAIN CAMPUS

**UNIVERSITY EXAMINATIONS
2022/2023 ACADEMIC YEAR**

SECOND YEAR SECOND SEMESTER EXAMINATIONS

**FOR THE DEGREE
OF
BACHELOR OF TECHNOLOGY EDUCATION
IN
ELECTRICAL AND ELECTRONIC ENGINEERING**

COURSE CODE: TEE 221

COURSE TITLE: ELECTRICAL MEASUREMENTS

DATE : 14TH APRIL 2023

TIME: 12:00 NOON - 2:00 PM

INSTRUCTIONS TO CANDIDATES

ANSWER QUESTION ONE AND ANY OTHER TWO QUESTIONS.
QUESTION ONE CARRIES 30 MARKS AND ALL OTHERS 20 MARKS EACH.

TIME: 2 Hours

MMUST observes ZERO tolerance to examination cheating

This Paper Consists of 4 Printed Pages. Please Turn Over. 

Question 1 (30mks)

- (a) *i)* List FIVE criteria for choosing the most suitable measuring instrument for a given application. [5mks]
ii) Define the following terms with regards to instruments: [5mks]
i) Calibration
ii) Traceability
iii) Mesurand
iv) Sensor
v) Calibration chain

- (b) A Rotary Variable Differential Transformer (RVDT) has the following data sheet information: [3mks]

Ranges:

$\pm 30^\circ$ linearity error $\pm 0.5\%$ full range

$\pm 60^\circ$ linearity error $\pm 2\%$ full range

Sensitivity: $1.1 (mV/V \text{ input})/\text{deg}$

Impedance: primary 750Ω , secondary 2000Ω

Input voltage: 3V

For an angular displacement input of 40° , determine:

- i)* the error due to non-linearity [2mks]
ii) the output voltage reading [1mk]
- (c) The bridge of Fig. 1 has the following components:

Arm AB: Unknown inductance L_1 with resistance R_1

Arm BC: $R_2 = 200\Omega$; Arm CD: $R_3 = 100\Omega$

Bridge balance is obtained when $L_4 = 50mH$ and $R_4 = 2\Omega$

- i)* Derive the equations for the unknown values L_1 , and R_1 [4mks]
ii) Determine L_1 , R_1 and Q factor for $f = 50 \text{ Hz}$. [3mks]

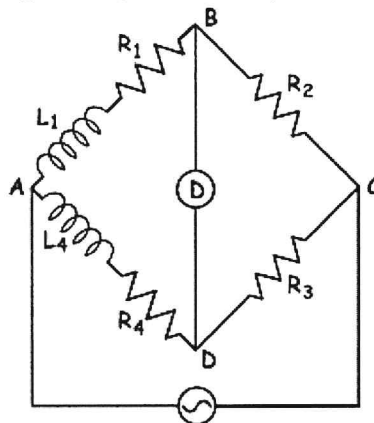


Fig. 1

- (d) State the function of the following parts of a cathode ray oscilloscope: [4mks]
i) Cathode ray tube
ii) Trigger Circuit
iii) Time Base Generator
iv) Aquadag coating

- (e) A voltmeter having a sensitivity of $1k\Omega/V$ reads 100V on its 150V scale when connected across an unknown resistor R_X in series with a milli-ammeter as shown in Fig. 2. Determine the value of R_X (in $k\Omega$) when the milli-ammeter reads 5mA. [5mks]


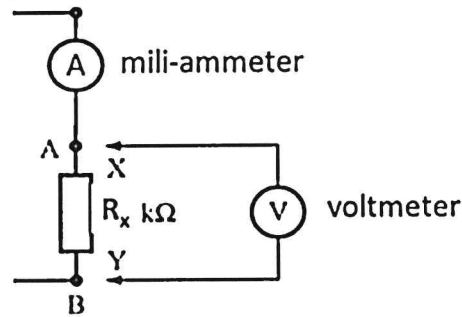


Fig. 2

Question 2 [20mks]

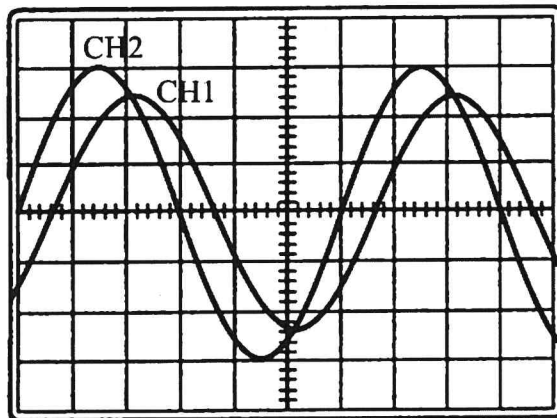- (a) Explain how a cathode ray oscilloscope (CRO) can be used to determine the dc voltage, rms voltage, current, phase difference and frequency of an ac signal. [8mks]
- (b) State FOUR differences between dual trace and dual beam oscilloscopes. [4mks]
- (c) The Fig. 3 shows the waveforms of a dual channel CRO with vertical sensitivity and timebase settings. [2mks]



Vertical sensitivity:
 $V_1: CH1 = 2V/div$
 $V_2: CH2 = 5V/div$

Timebase setting:
 $5ms/div$

Fig. 3

- i) Determine the period and frequency of V_1 and V_2 [2mks]
- ii) The peak to peak value of V_1 and V_2 [2mks]
- iii) The rms value of V_1 and V_2 [2mks]
- iv) The phase angle of V_1 relative to V_2 [2mks]

Question 3 (20mks)

- (a) With the aid of a circuit diagram, explain how Eddy current sensors can detect variations in thickness of a moving aluminium sheet. [6mks]
- (b) Four Piezoelectric crystals of charge sensitivity = $2pC/N$, area = $1cm^2$, 0.1 cm thickness and relative permittivity of 5, arranged in parallel under a platform and subjected to a force of 24N. Two metal electrodes measure changes in voltage in each crystal. Young's modulus of the crystal material is $E = 9 \times 10^{10}Pa$, and $\epsilon_0 = 8.85 \times 10^{-12}F/m$
- i) the voltage across the electrodes [3mks]
- ii) the change in crystal thickness [4mks]

- (c) A series circuit of Fig. 4 is connected to a 250V dc source. If R_2 is measured by voltmeters A and B having sensitivities of $500\Omega/V$ and $10k\Omega/V$ respectively. If both meters are used on the 150V range, determine the percentage error for each voltage measurement. [7mks]

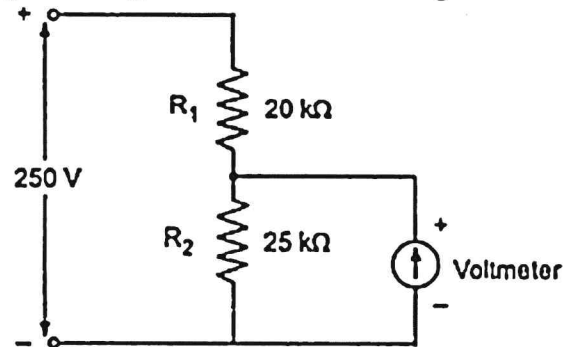


Fig. 4

Question 4 (20mks)

- (a) With the aid of a well labelled block diagram, describe how current, voltage and resistance measurements can be obtained with a digital multimeter. [8mks]
- (b) An R-L-C series circuit is tuned using a Q-meter. The oscillator frequency is 500kHz, shunt resistance is 0.5Ω , and variable capacitor set to 350pF. If the Q-value is 90, Calculate: [4mks]
- i) Effective inductance
 - ii) Coil resistance at resonance
- (c) Briefly describe with illustrations how Lissajous patterns can be used to determine the phase difference between two progressive waves. [8mks]

Question 5 (20mks)

- (a) The circuit in Fig. 5 is used to determine the inductance of the choke coil L_1, R_1 . When the bridge is fed from a source of 500Hz, balance is obtained under the following conditions:

$$R_2 = 2410\Omega \quad R_3 = 750\Omega \quad C_4 = 0.35\mu F, \quad R_4 = 64.5\Omega$$

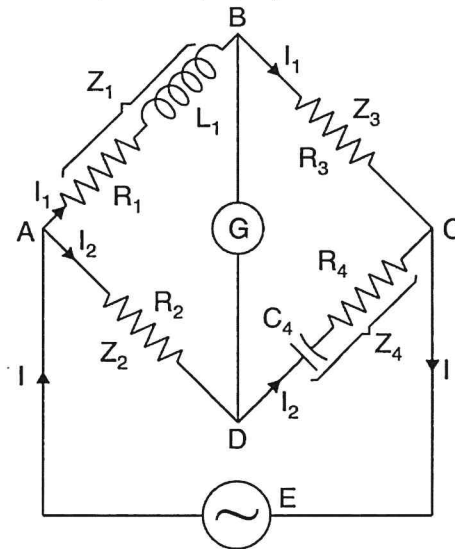


Fig. 5

- i) Derive the equations for the choke coil at balance conditions. [5mks]
 ii) Calculate the resistance and inductance of the choke coil. [3mks]

- (b) The specifications of a strain gauge bonded load cell are given as:

Modulus of elasticity (E)	$E = 120Mpa$
Load cell diameter	$3.5cm$
Strain gauge nominal resistance	600Ω
Gauge factor	$G = 3$
Bridge voltage supply	$V_s = 6V dc$

The strain gauge is aligned in the direction of tension and connected into a wheatstone bridge whose other arms have equal resistance of 300Ω . A galvanometer with current sensitivity of $5mm/\mu A$ and an internal resistance of 500Ω gives an offset of $3mV$. If the load cell is subjected to a compressive axial force, determine the following:

- i) Percentage change in gauge resistance due to the applied force [4mks]
 ii) The magnitude of the applied force on the load cell [4mks]
 iii) Galvanometer deflection [4mks]

