



**MASINDE MULIRO UNIVERSITY OF
SCIENCE AND TECHNOLOGY
(MMUST)**

MAIN CAMPUS

**UNIVERSITY EXAMINATIONS
2023/2024 ACADEMIC YEAR**

SECOND YEAR FIRST SEMESTER EXAMINATIONS

FOR THE DEGREE

OF

**BACHELOR OF SCIENCE
IN
MECHANICAL AND INDUSTRIAL ENGINEERING**

COURSE CODE: MIE 201

COURSE TITLE: CIRCUIT THEORY

DATE: THURSDAY 07/12/2023 TIME: 12:00 PM – 2:00 PM

INSTRUCTIONS TO CANDIDATES

ANSWER QUESTION ONE AND ANY OTHER TWO QUESTIONS.
QUESTION ONE CARRIES 30 MARKS AND ALL OTHERS 20 MARKS EACH.

TIME: 2 Hours

MMUST observes ZERO tolerance to examination cheating

This Paper Consists of 5 Printed Pages. Please Turn Over.

Question One (30 marks)

(a) Define the following terms:

- i) Mesh
- ii) Loop
- iii) Node

[3 marks]

(b) If $100\angle 0^\circ$ a.c is supplied to a circuit consisting of a 3Ω resistor and 4Ω capacitive reactance connected in series, determine the voltage across each element in the circuit. [3 marks]

(c) From fig. 1.1 below, use mesh analysis to find the mesh currents and voltage v_o . [5 marks]

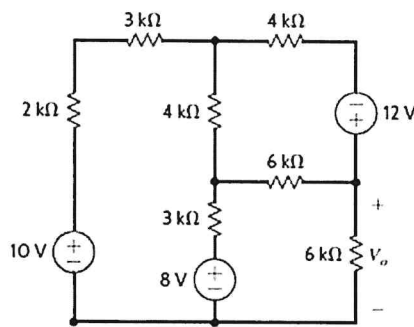


Figure 1.1

(d) With the help of illustrations, use the superposition principle to determine the value of i_x .

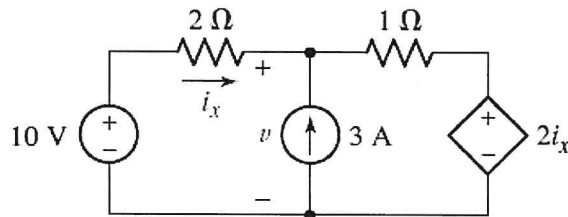


Figure 1.2

[6 marks]

(e) For the circuit in Figure 1.3 below, compute the voltage across each current source using the supernode method of analysis. [6 marks]

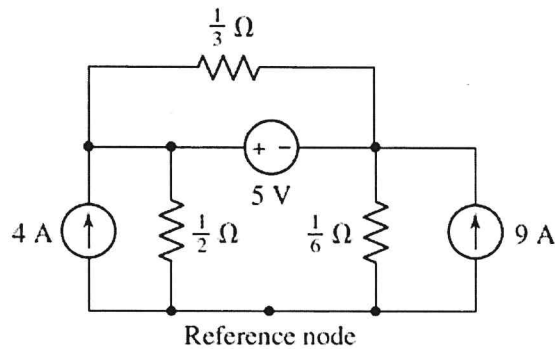


Figure 1.3

(e) A 230V, 50Hz a.c. supply is applied to a coil of 0.06H inductance and 2.5Ω resistance connected in series with a $6.8\mu\text{F}$ capacitor. Determine;

- i) Impedance [3 marks]
- ii) Current flowing through the circuit [1 mark]
- iii) Phase angle between current and voltage [2 marks]
- iv) Power factor. [1marks]

Question Two (20 marks)

a) Name and state Kirchoff's laws. [3 marks]

b) Determine the value of current in each branch when three resistors of values 3Ω , 2Ω and 4Ω are connected in parallel. The total input current fed to the resistors is $8A$. [4 marks]

c) In the circuit below, use resistance combination methods and current division to find i_1 , i_2 and v_3 . [7 marks]

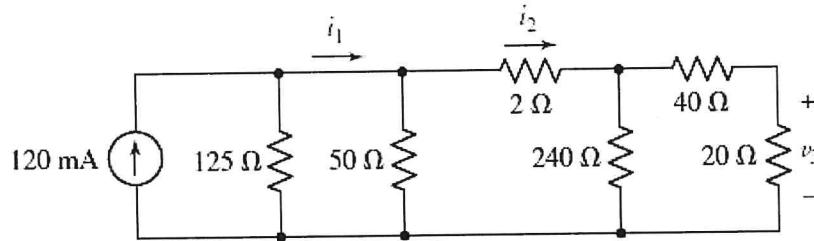


Figure 2.1

d) Determine the current i_1 in the circuit below using supermesh method. [6 marks]

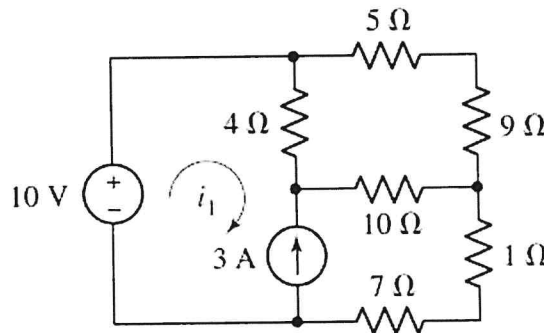


Figure 2.2

Question Three (20 marks)

(a) i) State Thevenin's Theorem. [1 mark]

ii) From Figure 3.1, use Thevenin's Theorem to find:

- I. V_{TH} and R_{TH} , [3 marks]
- II. the load current I_L flowing through the circuit, [2 marks]
- III. the load voltage across the load resistor in the circuit below. [2 marks]

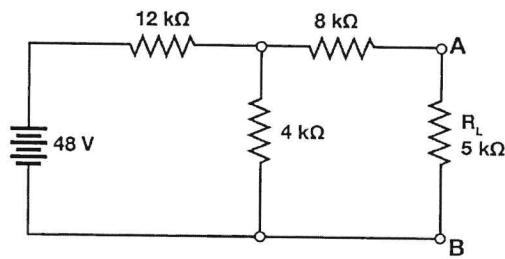


Figure 3.1

- (b) i) Explain mesh analysis. [2 marks]
 ii) Using the method explained above, determine the mesh currents in fig.3.2. [4 marks]

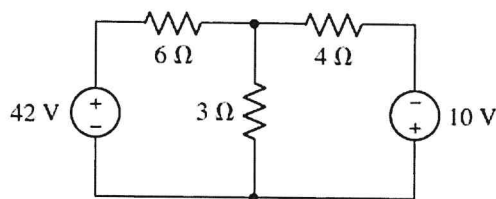


Figure 3.2

- (c) For the single-node-pair circuit below, find i_A , i_B and i_C . [6 marks]

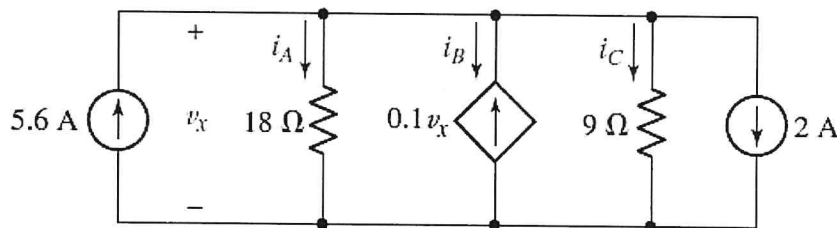


Figure 3.3

Question Four (20 marks)

- (a) The peak value of a sinusoidal voltage is 12V and it has a periodic time of 16milliseconds. Determine the;
- i) r.m.s value [1mark]
 - ii) average value [1mark]
 - iii) frequency of supply. [1mark]
- (b) A series RLC circuit containing a resistance of 12Ω , an inductance of 0.15H and a capacitor of $100\mu\text{F}$ are connected in series across a 100V, 50Hz supply.
- i) draw the circuit, [1 mark]
 - ii) calculate the total circuit impedance, [3.5 marks]
 - iii) determine the circuit current and voltage across each component, [2.5 marks]
 - iv) calculate the power factor, [1 mark]

v) draw the voltage phasor diagram.

[2 marks]

(c) For the circuit in fig. 4.1, calculate:

- i) the current I , [4.5 marks]
- ii) voltages v_R , v_L and v_C in phasor form, [1.5 marks]
- iii) the total power factor. [1 mark]

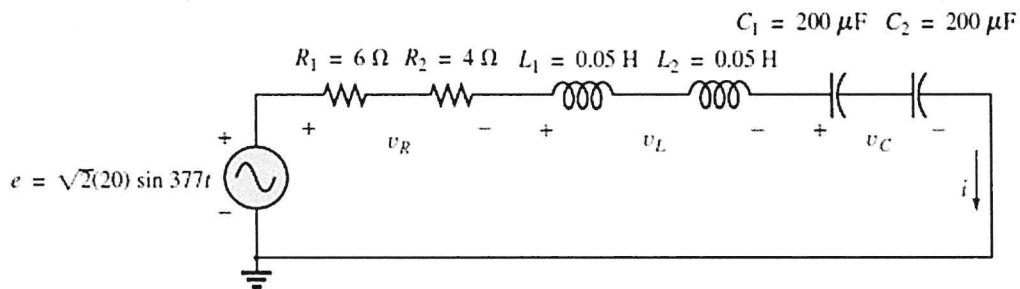


Figure 4.1

Question Five (20 marks)

a) Use mesh analysis to determine the current i_1 in the circuit of fig.5.1. [5 marks]

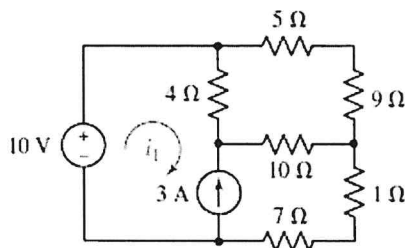


Figure 5.1

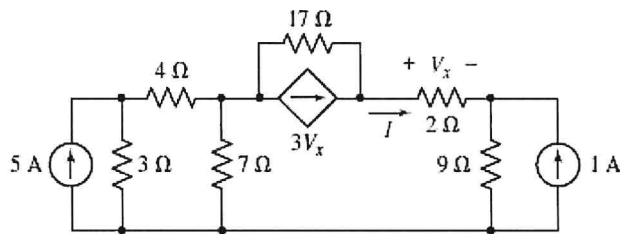


Figure 5.2

b) Calculate the current through the 2Ω resistor in Fig. 5.2 by making use of source transformations to first simplify the circuit. [5 marks]

c) Given that the elements $v_{s1} = -120 V$, $v_{s2} = 30 V$, $R_1 = 30 \Omega$ and $R_2 = 15 \Omega$ are all connected in series in a circuit, compute the power absorbed by each element. [5 marks]

d) Considering the network shown in fig.5.3 below, find the branch currents I_1 , I_2 and I_3 , using the supernode analysis method. [5 marks]

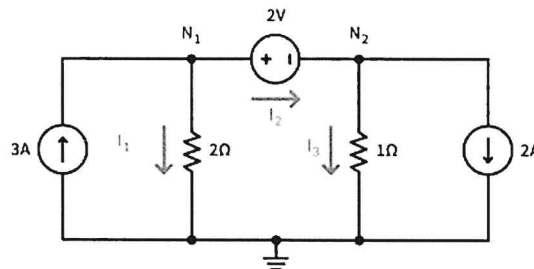


Figure 5.3

